


amateur radio

Vol. 38, No. 8

AUGUST, 1971

Registered at G.P.O. Mailroom, for
transmission by post as a periodical
Category 1

Price 30 Cents

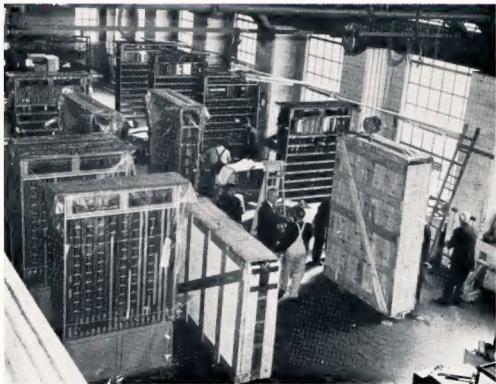

A & R OUTPUT TRANSFORMER

TYPE ED M16

Primary impedance, 8,000 ohms c.t.; ultra-linear screen taps, 43% turns; ult. secondary impedance, 2, 8 and 15 ohms; power rating, 10 watts; frequency response, plus or minus 2 db, 30 Hz. to 30 KHz.; overall size, 4 1/2 x 2 1/8 x 2 1/2 in.; mounting centres, 2 1/2 in.

Few Only! Price \$8.00. Postage \$1.

AMERICAN RECORDING TAPE

(New, in sealed boxes)

| | |
|---|--------|
| 1500 feet, 7-inch, Acetate, 1 1/2 mil. | \$3.50 |
| 1200 feet, 7-inch, Acetate, 1 1/2 mil. | \$2.50 |
| 1200 feet, 7-inch, Mylar, 1 1/2 mil. | \$3.00 |
| 1200 feet, 5 1/2-inch, Acetate, 1 mil. | \$2.20 |
| 1200 feet, 5 1/2-inch, Mylar, 1 mil. | \$2.50 |

Postage 10c.

METERS

MR2P METERS: square, face size 1 1/2-in., M/Hole 1 1/2-in., res. 90 ohms, 0-1, 0-25, 0-250, and 0-500 mA. Price \$5.50 nett.

MR2P METERS: 0-5, 0-10, 0-30, 30-30 Ampe. (Res. 50M/V). Price \$6.50 nett.

MR2P METERS: 0-15 volt DC, 0-30 volt DC. Price \$5.50.

MR2P METERS: 0-50, 0-100, 100-100, 0-500 uA. (Res. 900 ohms). Price \$6.75.

MO05 METERS: New. Face size 3 1/2-in., M/H 2 1/2-in., Res. 120 ohms, 0-1, 0-5, 0-10, 0-20, 0-50, 0-100, 0-500 mA. Price \$3.25 nett. Post. 20c.

MO05 METERS RES: 0-15, 0-30, 0-300 volt DC. Price \$3.40 nett. Postage 20c.

SWH 100 METER: Replacement. Price \$8.50. Postage 20c.

P25 "8" METER: Price \$6.50 nett.

P25 METERS: New. Face size 2 1/2-in., M/H 2 1/2-in., Res. 60 ohms, 0-1, 0-5, 0-50, 0-100, 0-500 mA. Price \$6.00 nett. Postage 20c.

MR2P METERS: New. Face size 3 1/2-in., M/H 2 1/2-in., Res. 120 ohms, 0-1, 0-10, 0-50, 0-100, 0-500 mA. Price \$6.75 nett. Postage 20c.

MR2P METERS: 0-50, 0-50, 0-100, 0-500 uA. Price \$6.20 nett. Postage 20c.

MASTER METERS: New. Model 821, Size 2 1/2-in., M/H 2 1/2-in., C/R 50-50 uA. Plain face. Price \$4.00 nett. Postage 20c.

MASTER METERS: New. Model 821 24F/400. Face size 3 1/2-in., M/H 2 1/2-in., C/R 1-1 mA. Plain face. Price \$3.70 nett. Postage 20c.

MASTER METERS: New. Model 212 24F/502, 0-10 volt AC. Face size 3 1/2-in., M/H 2 1/2-in., Price \$4.50 nett. Postage 20c.

GREEN CAP CONDENSERS

Values: 0.001, 0.0022, 0.0033, 0.0047, 0.0056, 0.0068, 0.0082, 0.01, 0.015, 0.022, 0.033, 0.039, 0.047, 0.056, 0.062 uF. Price 15c each.

Sizes: 0.1, 0.22, 0.33, 0.39, 0.47 uF. Price 15c each.

1 uF. (200v.w.), 2 uF. (200v.w.). Price 58c each.

RESISTORS

1/2 watt 8c each, 1 watt 15c each.

LAFAYETTE SOLID STATE HAGOOD COMM. RECEIVER

Five bands, a.m., c.w., a.s.b., Amstar and Short Wave, 150 to 400 KHz. and 550 KHz. to 30 Mhz. PET front end. Two mechanical filters. Huge dial. Product detector. Crystal calibrator. Variable RFQ. Noise limiter. 5 meter, 24 in. bandspread, 230v, a.c./12v, d.c., neg. earth operation. HF gain control. Size: 15 x 9 1/2 x 8 1/2 inches. Weight 15 lb. S.A.E. for full details.

Price \$199.50 nett.

LAFAYETTE HAGOOD, solid state, as above but Ham Band only. SSB-AM-CW. Price \$195 nett.

TRIO COMM. RECEIVER MODEL 9R-59DS

Four-band receiver covering 550 KHz. to 30 Mhz. continuous, and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valves plus 7 diode circuits. 4/8 ohm output and phone jack. SSB-CW-AM, AM, variable BFO. 5 meter, 24 in. bandspread dial, 1.455 KHz. audio output 1.5w., variable RF and AF gain control, 115/250v. a.c. mains. Beautifully designed. Size: 7 x 15 x 10 in. With instruction manual and service data.

Price \$178.50 including sales tax

Speaker to suit, type SP9D, \$15.30 incl. tax.

"REALISTIC" DX150 COMM. RECEIVER

Solid state, four bands covering 535 KHz. to 30 Mhz., fully transistorised, SW/CW/SSB/AM board-cut, 240v, a.s.c. or 12v, d.c. operation. Product detector for SSB-CW plus fast and slow a.v.c.; variable pitch a.f.c.; illuminated electrical bandspread, fully calibrated for Amateur bands, cascade r.f. stage; a.m. for r.f. and a.f.; a.s.b. stabilised; i.f. audio; illuminated 5 meter; built-in monitor speaker.

Price \$234.20 incl. tax

Matching speaker to suit, \$13.60

BROADCAST BAND TUNER

Locally made, Model 401 uses a shielded 3-stage I.F. Module with a single transistor mixer-osc. An AGC voltage is developed and applied to the 1st I.F. stage. High sensitivity is obtained with a ferrite rod, 8-in. long, 3/8-in. diam. Sensitivity: 150 uV; bandwidth: 8 KHz.; supply voltage: 9V; supply current: 5 mA.; audio output voltage: 0.5-1.0V; load impedance: not less than 47K. Operates in plastic box with dial. Ready to plug in. Price \$25.00 nett.

POCKET CRystal RADIO

Type ER22. Set complete. Price \$1.50.

A.C. ADAPTOR-BATTERY SAVER

Type P564—240 volts to 6 or 9 volts, 300 mA. \$12.50
Type P562—240 volts to 6 or 9 volts, 100 mA. \$9.50
Postage 30c

NEW HEADPHONES AND MIKE

Phones 8 ohms, Mike 25 ohms
Price \$15.75

THE NEW PEAK HS-250 SPEAKER

A completely new speaker designed to complement the best stereo equipment. Featuring a 10-inch two-way woofer and mid range cone speaker with ferrite magnet and a co-axial 2 1/2-in., horn-type tweeter. Resonant frequency 40 plus or minus 10 Hz.; frequency range, 40-20,000 Hz.; maximum power, 25 watts; nominal diameter, 10 inch; mounting diameter, 9-29/64 inch; voice coil impedance, 8 or 16 ohms; net weight, 55 oz. For the best in sound, fit the Peak HS-250.

Priced at a reasonable \$34.50. Postage 50c.

TELEPHONE INTER-COM. SETS

Telephone Inter-communication Set with signal bulb, two 12 batteries, ideal for children. Price \$6.75. Postage 30c.

EGG INSULATORS

For your Aerial. 8c each.

VARIABLE CONDENSERS

Single gang, 10-415 pF. Price \$2.20.

LOW PASS FILTERS

A "Cabana" Low Pass Filter will fix T.V.I. Cut-off frequency, 30 Mhz.; attenuation at 80 Mhz. better than 30 dB.; insertion loss, negligible. Impedance 50-72 ohms.

Price \$11.50. Postage 10c.

SOLID STATE STEREO AMPLIFIER

8 watts r.m.s. per channel, input for magnetic, crystal and ceramic type microphone, P.V. cartridges, tape recorder input and output, tuner input, stereo headphones jack.

Reduced to \$55.00. Postage \$1.20.

FIVE-CORE CABLE

5 x 5/976. Ideal for Intercoms., Telephones, etc. New. 100 yd. rolls, \$17 (postage 75c), or 200 yd.

STEREO HEADPHONES

Professional quality (well known brand). Large earpads, standard stereo plug, 6 ft. lead.

Price \$5.75. Postage 50c.

CRYSTAL CALIBRATOR NO. 10

Nominal range: 500 KHz. to 30 Mhz. 500 KHz. dial and 250 KHz./500 KHz. BFO. Provides heterodyne output in steps of 1 Mhz. Dial driven by machine cut strip gears, calibrated in 2 KHz. div. Easily read to 250 cycles. Output "spiked" approx. 1 sec. intervals, identifies beat note. Power requirements: 12v. DC at 0.3 amp., 250 volts at 15 mA. This is a precision instrument. Complete with crystal.

Price \$23.50

EXTENSION SPEAKERS

Type T330 Tubular Extension Speakers, 8 ohms, new. Complete with lead and two plugs 2.5 and 3.5 mm. Price \$4.30. Postage 20c.



RADIO SUPPLIERS

323 ELIZABETH STREET, MELBOURNE, VIC., 3000

Phones: 67-7329, 67-4286

All Mail to be addressed to above address

Our Disposals Store at 104 HIGGETT ST., RICHMOND (Phone 42-8136) is open Mondays to Fridays, 10.30 a.m. to 5.0 p.m., and on Saturdays to midday.

We sell and recommend Leader Test Equipment, Pioneer Stereo Equipment and Speakers, Hitachi Radio Valves and Transistor Radios, Kew Brand Meters, A. & R. Transformers and Transistor Power Supplies, Ducon Condensers, Welwyn Resistors, etc.

amateur radio

JOURNAL OF THE WIRELESS INSTITUTE OF AUSTRALIA. FOUNDED 1910



AUGUST, 1971

Vol. 39, No. 8

Publishers:

VICTORIAN DIVISION W.I.A.
Reg. Office: 478 Victoria Pde., East Melbourne,
Vic., 3002.

Editor:

K. E. PINCOTT VK3AFJ

Publications Committee:

R. Doris VK3ZU
Ken Gillespie VK3GK
Harold Hepburn (Secretary) VK3AFD
Peter Ramsay VK3ZWN
W. E. J. Roper VK3ARZ

Circulation—

Jack Kelly VK3AFD

Draughtsmen—

John Blomch VK3ZOL
John Whitehead VK3YAC

Enquiries:

Mrs. BELLAIRS, Phone 41-3535, 478 Victoria
Parade, East Melbourne, Vic., 3002. Hours:
10 a.m. to 3 p.m. only.

Advertising Representatives:

TECHNICAL NEWS PUBLICATIONS
21 Smith St., Fitzroy, Vic., 3065. Tel. 41-4962.
P.O. Box 108, Fitzroy, Vic., 3065.

Advertisement material should be sent direct
to the printers by the first of each month.

Hamads should be addressed to the Editor.

Printers:

"RICHMOND CHRONICLE." Phone 42-2419.
Shakespeare Street, Richmond, Vic., 3121.



All matters pertaining to "A.R." other than
advertising and subscriptions, should be
addressed to:

THE EDITOR,

"AMATEUR RADIO,"

P.O. BOX 36,

EAST MELBOURNE, VIC., 3002.



Members of the W.I.A. should refer all enquiries regarding delivery of "A.R." direct to their Divisional Secretary and not to "A.R." direct. Two months' notice is required before a change of mailing address can be effected. Readers should note that any change in the address of their transmitting station must, by P.M.G. regulation, be notified to the P.M.G. in the State of residence; in addition, "A.R." should also be notified. A convenient form is provided in the "Call Book".

CONTENTS

Technical Articles:—

| | Page |
|--|------|
| Angle Modulation—Lecture No. 14B | 3 |
| Home Station Antenna for 160 Metres: Part Four—Practical Application | 13 |
| P.e.p., Average Power, and Related Matters | 6 |
| Practical V.h.f. and U.h.f. Coil-Winding Data | 7 |
| V.h.f. Meteor Scatter Propagation | 11 |

General:—

| | |
|--|----|
| Antarctica Research | 15 |
| Australian Flying Corps No. 1 Squadron in Egypt 1917 | 16 |
| Book Review: "Understanding Amateur Radio" | 10 |
| Correspondence | 21 |
| DX | 22 |
| Federal Awards | 22 |
| Federal Comment: An Open Reply to an Anonymous Letter | 2 |
| Federal Contest Committee | 20 |
| Golden Jubilee | 20 |
| Indonesia Licensing | 15 |
| Licensed Amateurs in VK | 15 |
| New Call Signs | 17 |
| Obituary | 15 |
| Observation Post | 20 |
| Overseas Magazine Review | 19 |
| Prediction Charts for August 1971 | 19 |
| Repeater News | 23 |
| Silent Keys | 24 |
| SPX Bulletins | 21 |
| VHF | 23 |
| W.I.A. D.X.C.C. | 24 |
| 3 Squadron Amateurs at Richmond, N.S.W., 15th July, 1940 | 16 |

COVER STORY

Industry, as well as Radio Amateurs, uses relays for switching purposes. Here 22 relay racks are being pre-wired for signalling of Melbourne railway yard. Each rack holds 231 transistor radio size relays.
(Block by courtesy of V.R.I.)

AN OPEN REPLY TO AN ANONYMOUS LETTER

"Michael Owen, VK3KI,
Dear Sir,

Having perused Ron's (VK3RN) correspondence item in the July issue of "Amateur Radio," I can only fully agree with his findings.

The Institute is seeking an increase in membership—that is the impression I get from the various articles I read. My personal advice is, you are not seeking in the right areas. There are many who would join the organisation if it would at least attempt to try to do something for them. I have spoken with Limited licensees on the question of the W.I.A., but they have said that they would not join. They feel that the Institute serves only one class, and that it has done nothing towards fighting for better frequency allocations for them.

The Institute has now worsened their image in their sight, in as much that you are willing in principal to allow an unskilled Novice on the h.f. bands, and the Limited licensee well knows of your opposition towards his gaining a little extra. If these people were allowed to operate on some of the h.f. bands it might liven it up a bit, because they are quite dead at the moment. As far as I am concerned these people in most cases are more than technically qualified—the greater percentage being employed in the electronic industry as engineers and advanced technicians.

Close your eyes if you dare—but let me warn you that it is in danger of starting an organisation* totally divorced from you, then it will be too late for you to make amends.

—A VERY FULL-UP CALL

*This could [be] closer than realised."

Dear Mr. Anonymous Letter Writer,

Unfortunately, as you did not put your name or address on your letter, I cannot reply to you personally. However, as I think you have raised some important issues, I think that it is proper to reply to your letter through this magazine. I hope that you do not mind.

At the outset, I would like to thank you for your interest in writing to me expressing your opinion. I think that is very good; it is really what the Institute is all about. It's task is to represent the Amateur Service in our country and obviously it can't do this without knowing what Amateurs think. Of course I think I should also point out that the anonymous letter is usually the least effective way of expressing views.

Having said that, may I join issue with you, Mr. Anonymous Letter Writer, on a number of things that you say in your letter as I am afraid that you have been misinformed on a number of points.

You are right, of course, when you say that the Institute seeks an increase

in membership. The higher the percentage of licensees that are members of the Institute, the more representative the organisation is of the Amateur Service and, at the same time, the more effective can be its representation. That is why I think that it is in all our interests for as many Amateurs as possible to be members of the Institute.

But then you go on to say that you have spoken to many Limited licensees but that they feel that the Institute represents only one class of licence and has done nothing towards fighting for better frequency allocations for them. Your comment really surprises me. As I was a Limited licensee myself for ten years prior to 1967, I have always had a particular interest in the v.h.f. spectrum.

Mr. Anonymous Letter Writer, you seem to have overlooked the fact that the Limited licence was only introduced because of the representations of the Institute. You also overlooked the fact that a major portion of the Federal Council and Federal Executive's time in the last two years has been devoted to the International Telecommunications Union Space Conference which, as I write to you, is now in session in Geneva. This Conference is of great interest to the v.h.f. operator and it is possible that it could substantially affect his operating rights and privileges. You overlook also, that as a result of what the Institute has done, our country is one of the countries at this Conference that has taken up the cause of the Amateur Service. You also overlook the fact that as a member of the Region 3 Association (which, incidentally, was formed as a result of the initiative of the Institute in 1968) the Institute is a substantial contributor to the costs of sending a representative, Tom Clarkson, 2L2AZ, of New Zealand, to Geneva as a member of the International Amateur Radio Union Observer team. There, he is our special representative at the Space Conference.

You asked for "better frequency allocations". Yes, I know all about the 6 metre band—you cannot win them all. But really, are you serious in seeking more v.h.f. spectrum? I have not noticed an overcrowding problem on either the 144-148 MHz. allocation or the 420-450 MHz. allocation. Have you? I am not sure that your letter makes your complaint completely clear.

I think you really mean that Limited licensees should be permitted to operate on bands below 52 MHz. Many people will agree with you, but I rather think that more will disagree with you. Of course, if you are a member of the Institute, it is open to you to attempt to persuade the other members of the Institute to adopt a long term policy in relation to the Morse qualification requirement.

But, of course, the simple fact is that this is not just a matter for the Australian Post Office. Australia, as a

member of the International Telecommunications Union, is bound by the I.T.U. Convention, an international agreement between countries. That agreement specifies that a Morse qualification is required for Amateurs licensed to operate below 144 MHz., though in fact in Australia, this qualification is only required below 52 MHz.

I am afraid that you have completely misconceived the present position in relation to Novice licensing. You also seem to think that I am personally "pushing" the Novice licence proposals. I am not. Neither I nor the Federal Executive have expressed any view at all on this matter. The policy of the Institute at this time is not to advocate the issue of a Novice type licence, but the Institute is having another look at this policy. The Federal Council has sought a report from a committee formed for the purpose and the Divisions are now seeking the views of members generally. That is the reason that I am not expressing any view on the question of a Novice licence. As Federal President, I feel that on this matter I should not, in any way, attempt to influence members to my particular view at this time.

If, Mr. Anonymous Letter Writer, you are a member (and you do not make this clear), then you can and I suggest **should**, take part in Institute affairs by expressing your view. As I said at the outset, that is what the Institute is all about. I agree with you that we do need more Amateurs on the h.f. bands. I think we need more Amateurs on all bands, but I believe that the Institute has to be realistic. We cannot, even if we want to (and I do not suggest that we do), just go and change the International Regulations. The Institute can, however, make it easier and more attractive for the Limited licensee to obtain a full licence. Do you remember, Mr. Anonymous Letter Writer, that the Morse code speed used to be 14 words per minute? It was the Institute that successfully sought a reduction of this speed to 10 words per minute.

No, Mr. Anonymous Letter Writer, I do not think that neither I nor the Institute has to make amends to the Limited licensees. We are not perfect and certainly we cannot expect all our members to be in agreement on every issue all the time, but I do think that the Limited licensee has no basis for thinking the Institute is not representing him.

Indeed, it may well be that the thinking Limited licensee, who knows the real facts, could conclude that he should be a member of the Institute because of what it is now doing for him and because, perhaps, it could do even more, given more support by Limited licensees.

Yours sincerely,

Michael J. Owen, VK3KI,
Federal President.

ANGLE MODULATION

LECTURE No. 14B

C. A. CULLINAN,* VK3AXU

Using sine waves, it is possible to illustrate the differences between amplitude, frequency and phase, and this has been done in Fig. 1.

Fig. 1a shows a single sine wave at three different amplitudes.

Fig. 1b shows three sine waves of the same amplitude and phase, but differing in frequency.

Fig. 1c shows three sine waves of the same frequency and amplitude, but differing in phase.

These three figures should be studied closely.

FREQUENCY MODULATION

When using an audio frequency voltage to produce f.m., it is the amplitude of the voltage which causes the carrier frequency to shift or deviate symmetrically from its assigned frequency pre-emphasis of 75 micro-seconds. However, in Australia for television sound the maximum deviation is ± 80 KHz. and audio frequency pre-emphasis of 50 micro-seconds.

In the U.S.A. for f.m. broadcast stations the maximum deviation is ± 75 KHz., and audio frequency pre-emphasis of 75 micro-seconds, however for television sound the maximum deviation is ± 25 KHz. with an audio frequency pre-emphasis of 75 micro-seconds.

Digressing for a moment; in the Australian mobile radio-telephone services in the frequency bands 70-85 MHz. and 156-174 MHz., as from 30th June, 1969, the maximum deviation permitted for angle modulated stations has been ± 5 KHz. (International maritime mobile u.h.f. radio-telephone and existing P.M.G. subscriber services were excluded.) The reduction of deviation to ± 5 KHz. was made to enable 30 KHz. channeling of mobile stations so that more "speech" type stations could be accommodated in the available spectrum space. However, in January 1970 the demand for f.m. mobile services was becoming so great that stations in the same area had to share a common carrier frequency.

It is proposed to use the Australian standards in the remainder of this lecture to avoid confusion. This means that the loudest passage of, say, a musical concert would cause the carrier to deviate ± 50 KHz. Thus the maximum applied audio frequency modulating voltage produces the maximum frequency deviation of the carrier whilst the carrier amplitude remains constant.

This is in direct contrast to amplitude modulation where the carrier frequency remains constant but the amplitude varies.

Thus if one of the sine waves shown in Fig. 1a was applied simultaneously to an f.m. transmitter and an a.m. one it would produce a certain amount of frequency deviation in the f.m. transmitter and a certain amount of ampli-

Continuing the series of lectures by C. A. Cullinan, VK3AXU. at Broadcast Station 3CS for students studying for a P.M.G. Radio Operator's Certificate.

tude variation in the a.m. transmitter. Then each of these characteristics would be varied if either of the other waves of Fig. 1a was to be substituted.

Furthermore, it must be realised that in an f.m. transmitter the frequency deviation depends entirely on the amplitude of the modulating wave, not on its frequency, thus if we take two frequencies at random, say 200 Hz. and 3,000 Hz., the carrier frequency deviation depends on the amplitudes of these frequencies.

Now in speech, music and sounds produced in nature, it is almost impossible to find a sustained sine wave, as almost all sounds are made up of many waves and produce complex waves. Our radio and television receivers recover such complex waveforms from the transmitted signal and the loud-speaker converts this into the motion of particles of the air, to produce sound waves which our ears can register and understand.

However, so far in this discussion of f.m. we have described only the manner in which an audio frequency voltage, sine wave or complex, causes deviation of the carrier frequency and

this, on its own, would not enable intelligent signals to be transmitted as we must recover, in our receivers, the frequency components of the modulating wave.

Therefore, in an f.m. transmitter the rate or frequency with which the deviation takes place is determined by the frequency of the modulating voltage. Referring back to our previous example, let us assume that both the 200 Hz. and the 3,000 Hz. waves are at the same amplitude, then each, if applied separately, will produce the same amount of deviation, but in the first case the rate of deviation will be 200 times per second and in the second case it will be 3,000 times per second.

In the receiver the rate of deviation is recovered as the various audio frequencies and the deviation is recovered as the amplitude or volume level of the signal.

In Fig. 2a we see an audio frequency voltage in the form of a single sine wave applied to an f.m. transmitter operating at 100 MHz. and of sufficient amplitude to produce 10% deviation. It will be observed that the carrier frequency varies above and below its unmodulated value of 100 MHz. by an amount which is directly proportional to the amplitude of the modulating voltage; in this case ± 5 KHz.

The frequency deviation is known as f_d , and as mentioned earlier, its maximum excursion is 50 KHz. This does not mean that the total bandwidth for full modulation is 100 KHz., but is the value of twice the modulating frequency

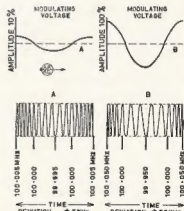
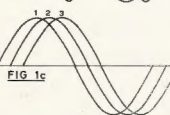
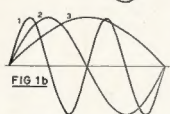
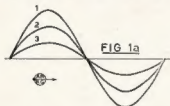


Fig. 2 is not drawn for any particular audio frequency. Therefore if the audio frequency is, say, 100 Hz. then time is 1/1000th second, for 1,000 Hz. time is 1/1,000th second, and for, say, 15 KHz. time is 1/15,000th second.

Fig. 2 shows that the deviation is entirely dependent on the amplitude of the modulating voltage, not of frequency.

It is the frequency of the modulating voltage which governs the rate at which the deviation takes place.

Modulation index equals deviation of f.m. carrier divided by audio frequency producing this deviation.

* 6 Adrian Street, Colac, Vic., 3250.

SIDEBAND ELECTRONICS ENGINEERING

To the list of Transceivers, available at reduced prices, are to be added two products of K.W. ELECTRONICS LTD. of England. Solidly built sets, as to be expected from British manufacture, the ATLANTA five-band Transceiver (a copy of the SWAN 500) and the KW2000B (which is built along the lines of the Collins KWM2), similar in appearance with the 160 metre band added—the only Transceiver with that band covered! Both sets will arrive in August with their own AC power supply-speaker units, but in limited quantities. The same applies to the YAESU MUSEN Transceivers listed, so better hurry to profit from the special offers and low prices.

—Arie Bles

YAESU MUSEN

| | |
|--|-------|
| FT-101 AC/DC Transceiver, with the latest modifications, improvements, etc. | \$520 |
| FT-200 with heavy duty power supply | \$350 |
| FT-DX-400 AC Transceiver de luxe | \$425 |
| FT-DX-401 AC Transceiver super de luxe with CW filter, WWV, etc. | \$465 |

K.W. ELECTRONICS

| | |
|---|-------|
| ATLANTA 500 watt P.E.P. Transceiver, with AC supply unit | \$500 |
| KW-2000-B Six-band Transceiver, with AC supply unit | \$550 |

ELECTRONIC KEYERS

| | |
|--|------|
| KATSUMI, Model EK26, with built-in monitor, 240V. AC operation, keying paddle attached, fully or automatic operation, with switching transistors and keying relay, speeds up to 65 w.p.m. | \$60 |
|--|------|

ANTENNAS

| | |
|---|-------|
| Hy-Gain TH6DXX Master Tri-bander | \$220 |
| Hy-Gain 14AVQ Vertical | \$52 |
| Hy-Gain Hy-Quad, Tri-band Cubical Quad with gamma matches for single co-ax. feedline | \$130 |
| MOSLEY TA33Jr Tri-band Junior Beam | \$105 |
| Mosley MUSTANG Tri-band Beam, 1 kW. power | \$130 |
| NEUTRONICS 4-BTV 4-band Vertical | \$60 |
| WEBSTER and MARK Helical Mobile Whips | \$55 |

VALVES AND TUBES

| | |
|---|--------------|
| CETRON 572-B 150 W. zero-bias linear amplifier triodes | \$45 |
| EIMAC 3-500-Z zero-bias triodes | each \$37.50 |
| All types of Transceiver Valves—you name them, we have them in stock. | |

DIGITAL CLOCKS

| | |
|---|------|
| Caslon 24-hour, date and day of the week, 240V. AC | \$25 |
|---|------|

CRYSTALS

| | |
|---|--------|
| FT-241 type, all Channels 0 to 70, 375 to 415 KHz. per box of 80 Crystals | \$15 |
| Sets of six FT-241 matched for filter use, 375 to 450, and 470 to 515 KHz. per set | \$7.50 |

MIDLAND PRODUCTS

| | |
|---|--------------|
| The Type 13-710 one-watt Transceiver, soon also available with crystals for 28.1, 28.2, 28.3, 28.4 or 28.5 MHz. for the same price | each \$37.50 |
| Type 23-135B Field Strength Meter, with five ranges, tunable from 1 to 200 MHz., with telescoping whip | \$10 |
| Type 23-136 SWR-Power Meter, dual meters 100 micro-amp., very sensitive for low power but good for 1 kW. maximum, up to 175 MHz., reads forward and reflected power simultaneously, 52 ohm impedance | \$20 |
| Type 23-126 SWR Meter, standard single meter type, 52 ohm impedance, with whip for field strength metering | \$12 |
| PTT Dynamic Hand Microphone, steel case, 50K ohm impedance, excellent voice quality, no rocking armature type, with coiled cord and mobile use clip | \$10 |
| Table Model Dynamic Microphone, with PTT bar or lock switch, 50K ohm imped., a quality bargain at | \$15 |
| Same Table Microphone with built-in two-stage pre-amplifier, adjustable for up to 50 dB. amplification | \$25 |
| Co-ax. Connectors, Midland types PL-259, SO-239 females with or without flanges, PL-258 double-ended female; per connector | each 75c |
| Co-ax. Inserts for PL-259 for thinner co-ax. cable; each | 20c |
| Midland 5-watt Base Station Transceivers, eight-channels, 240V. AC, fully P.M.G. approved for 27.880 MHz. operation, with S meter and power-output metering, including PTT microphone, with switch to be used as 3-watt public address amplifier into separate speaker(s). All inclusive, only | \$100 |

TRANSFORMERS

Still a few types of the old stock of new NATIONAL Transformers left!

All prices quoted are net, cash with order, subject to alteration without prior notice, sales tax included in all cases. Postage, freight and insurance are extras, and transformers are heavy!

SIDEBAND ELECTRONICS ENGINEERING

Proprietor: ARIE BLES

Telephone: Springwood (STD 047) 511-394,
not part of the Sydney telephone exchange

P.O. BOX 23, SPRINGWOOD, N.S.W., 2777

plus double the deviation; i.e. if a modulation frequency of 15 KHz. is applied to give full frequency deviation, then the bandwidth will be $(2 \times 15) + (2 \times 50) = 130$ KHz. This is shown in Fig. 2b which illustrates an audio frequency modulating voltage producing a deviation of ± 50 KHz.

Note that Figs. 2a, and 2b are not drawn to the same scale, as 2b would be ten times the size of 2a if drawn to the same scale.

The centre frequency of 100 MHz. has been used for ease in explanation. In Australia there would not be any angle modulated transmitter on this frequency, the nearest to it being the sound transmitter of television channel 4 where the centre frequency is 100.75 MHz.

The effect of an inductance on an alternating current is to cause the current to lag 90° behind the voltage and the amount of the current will be dependent on the frequency of the voltage, the amplitude of the voltage and the amount of the inductance. Should the frequency be held constant then there will be an increase of current as the inductance is decreased.

This may be restated by saying that if the inductance is held constant, then the current will increase as the frequency decreases. Mathematically this may be expressed as: $I = E \div (2\pi fL)$.

It will be remembered from Ohm's Law that when two resistances are connected in parallel then the resulting resistance is less than the value of the lowest resistance.

A similar state of affairs exists if two inductances are connected in parallel as the resulting inductance will be less than either of the two inductances.

Inductances are impedances, mainly reactive, and we can state the parallel resistances formula for impedances like this: $Z = (Z_1 \times Z_2) \div (Z_1 + Z_2)$.

We have stated above that one property of an inductance is to cause the current in an a.c. circuit to lag behind the voltage and it is proper to consider that anything that can cause the current to lag behind the voltage may be considered to have the property of an inductance even if physically it does not resemble an inductance in any manner.

We also know from a.c. theory that the effect of a capacitance in an a.c. circuit is the opposite of an inductance, that is, a capacitance causes the current to lead the voltage.

As mentioned earlier, a valve may be connected in such a manner that it appears to be a reactance and the circuit may be arranged so that this reactance can be either positive or negative.

Fig. 3 shows the circuit of a reactance valve modulator. This reactance valve modulator will appear as an inductive reactance.

Here briefly is the manner in which this occurs.

The resistance R is made very large in comparison to the capacitive reactance of condenser C and as a result of this, r.f. current from the oscillator tank circuit passing through R and C is essentially in phase with the voltage across the oscillator tank. This means

that the current through condenser C is in phase with the voltage across the oscillator tank circuit.

Going back to a.c. theory, we remember that the voltage across condenser C will lag behind the current by 90° and it is this voltage which is applied to the grid of the valve. Now as the voltage on the valve grid varies so does the valve's plate current in phase with the grid voltage; i.e. whenever the grid voltage decreases so does the plate current and vice-versa.

It was stated above that the voltage across C is 90° out of phase with the current (lagging) and as the valve plate current is in phase with the grid voltage (across C), then the valve plate current lags behind the oscillator tank current by 90° ; therefore the valve is, in effect, an inductance in parallel with the oscillator tank circuit.

The amount of plate current drawn by the reactance valve, and thus its effective inductance, depends on the grid bias of the valve. If the bias is changed by applying an audio frequency voltage to the grid of the valve, the plate current will vary in accordance with this voltage and so will the effective inductance of the valve. As this inductance is in parallel with the oscillator tank inductance, the frequency of the oscillator can be varied in amplitude in accordance with the amplitude of the audio frequency voltage and the rate at which the oscillator frequency is varied will be governed by the actual frequency of the a.f. voltage at the grid of the modulator valve.

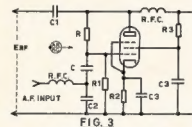


FIG. 3
REACTANCE VALVE MODULATOR
C and R, phase shift network; C1, d.c. blocking condenser; C2, C3, by-pass condensers; R1, grid leak; R2, cathode bias resistor; R3, across dropping resistor; R.F. input voltage from oscillator tank circuit.

Thus an audio frequency has brought about frequency modulation of an oscillator valve by changing the inductance of the oscillator tank circuit.

If the condenser C and the resistance R in the reactance valve circuit are inter-changed and the resistance of C is made far greater than the resistance of R, then the r.f. current flowing through C and R will be 90° ahead of the r.f. voltage across the oscillator tank circuit and the reactance valve will appear as a capacitive reactance.

Therefore with an audio frequency voltage impressed on the grid of the reactance valve frequency modulation of the oscillator valve will be obtained by varying the capacitance of the oscillator tank circuit.

In practice the phase shifts may not be exactly 90° and in practical transmitters two reactance valves may be

used in push-pull, also negative feedback may be employed.

The amount of frequency deviation that can be obtained is not very great so that it becomes necessary to use considerable frequency multiplication to get the necessary frequency deviation.

There is another way in which angle modulation differs from amplitude modulation. An amplitude modulated carrier frequency cannot be multiplied successfully because any multiplication also multiplies the sidebands and renders them unintelligible.

It is quite easy to amplitude modulate a carrier and beat or heterodyne it to another frequency because only the carrier frequency is changed. This is what happens in a superheterodyne receiver where an incoming amplitude modulated signal is heterodyned to an intermediate frequency for amplification. It does not matter if the a.m. signal is double sideband with carrier, d.s.b., s.s.b., or i.s.b.

However, an angle modulated carrier may be multiplied as well as heterodyned without difficulty.

Let us refer back to Fig. 2. The centre frequency is 100 MHz. and the deviation is ± 50 KHz. Suppose we have an oscillator on 4 MHz. and reactance valve modulates it to give a frequency deviation of ± 2 KHz. To put the carrier on 100 MHz. it will be necessary to multiply the 4 MHz. frequency twenty-five times and this will automatically increase the deviation frequency of ± 2 KHz. to ± 50 KHz. Actually a multiplication factor of twenty-five could be awkward to obtain but was chosen to make our figuring easy.

As mentioned previously, the development of solid-state devices has resulted in transmitters in which the full deviation can be obtained at the carrier frequency by direct modulation of the oscillator which is at the carrier frequency (d.c.f.m.), and as a result of this the reactance valve modulator is rapidly dropping out of favour.

One of the problems which occur when frequency modulation is derived by modulation of the oscillator is that the centre frequency of the oscillator may drift. (It is not usual to frequency modulate a quartz crystal oscillator although it can be done—if a crystal oscillator is to be used, it is more usual to employ phase modulation.)

There are several methods of keeping the oscillator on its centre frequency, despite modulation, and there are several variations of these methods. In one method a sample of r.f. from the oscillator is divided down to a lower frequency and compared to a quartz crystal oscillator. Stated simply, if the divided frequency and that of the crystal are the same, then there will not be any difference between them. However, if the modulated oscillator drifts then there will be a difference between the divided signal and the quartz crystal frequency. This difference can be extracted to determine if it is higher or lower than the crystal frequency, then amplified. It may then be fed to a two-phase electric motor which is geared to a small variable

(Continued on Page 16)

P.e.p., Average Power, and Related Matters*

JAMES N. THURSTON, W4PPB

When an Amateur picks up a catalogue and looks at the power ratings of transmitters or amplifiers, it is more than likely that he will be confused, dismayed or possibly convinced that manufacturers have double or triple standards when it comes to power ratings. It is my purpose to clear up some of this confusion by discussing what some of the power ratings actually mean.

The maximum input power that a transmitter can run is usually determined by the final amplifier stage. On one hand we have the problem of not exceeding the tube capabilities, especially with respect to dissipation. With the linear amplifiers that are used in s.s.b. service, the maximum input is also limited as to the amount of distortion in the form of flat-topping that can be tolerated.

As explained in the A.R.R.L. Handbook, p.e.p. is an abbreviation for peak envelope power. P.e.p. is the power resulting with key-down operating conditions, or conditions that occur on the highest audio peaks. Thus, a p.e.p. input of 100 watts means that the d.c. input power to the amplifier would be 100 watts if the maximum allowable steady signal were applied, if someone whistled the maximum allowable sine wave into the microphone, or if a two-tone input were applied so that the peaks would just reach 100 watts. In many linear amplifiers (except class A), the d.c. input power rises from a small value at zero signal input to a maximum with the drive signal applied. Also, if the amplifier is truly linear, the input signal and the output signal must be linearly related.

Perhaps some numerical examples will help to illustrate some common situations. For our first example let us suppose that we have an a.m. signal with a carrier rating of 100 watts. Assume that single-tone, sinusoidal modulation is applied so as to modulate the carrier 100%. Since the carrier amplitude doubles on modulation peaks with amplitude modulation, the input power on peaks will be four times the carrier value. Thus the amplifier must have a p.e.p. input rating of 400 watts. The average input power with 100% modulation will be 150 watts, since 50 watts will be supplied for the side frequencies. With a final amplifier stage that is 90% efficient, there will be 75 watts of power dissipated in the final amplifier tubes, for a steady 100% modulated input. Thus this final stage has the dual requirement of being able to handle a p.e.p. input of 400 watts without distortion and also of being capable of dissipating about 75 watts without overheating. Of course voice waveforms are not sine waves, and the average power figures given above are conservative as far as voice input is concerned.

As a second example, let's use the same amplifier rated at 400 watts p.e.p. and use it for s.s.b. operation. If a single-tone input is used, the peak power input of 400 watts which would result could not be permitted to continue for more than a very few seconds. The reason being that the input of 400 watts would mean that the tubes would be dissipating 200 watts, which is beyond the 75-watt dissipation rating previously assumed. Fortunately, however, the nature of the human voice with its pauses and variations in amplitude is such that the average power input is far less than the peak power input. An average power dissipation rating of 75 watts should normally be more than adequate for a 400-watt p.e.p. s.s.b. input. The ratio of p.e.p. ratings to average dissipation ratings is often six or eight to one, which explains why many s.s.b. transmitters must be tuned quickly, and why many are tuned up at a low level.

As a third example let us take a linear amplifier that is used for c.w. operation. In effect, it is either full on or full off, depending upon whether the key is up or down. Obviously the transmitter is heating up when the key is down, and is cooling off when the key is up. The duty cycle is a measure of the percentage on time, and is considerably less than 50% for average c.w. operation. Such factors as pauses, spaces between dots and dashes, and letters and words are of course taken into consideration. Usually a linear amplifier will run hotter with a given maximum input on c.w. than it does on s.s.b. because the usual duty cycle for c.w. is greater than it is for s.s.b. Because of this, many transmitters have c.w. ratings which are about 75% of their s.s.b. ratings.

As an example, the word "amateur" followed by a standard 7-unit space,

has a duty cycle of slightly less than 50%. This is probably higher than that of an average text. A 40% duty cycle, with a maximum input of 400 watts, would mean an average power input of 160 watts, and a plate dissipation of 80 watts at the 50% efficiency level previously assumed. Under such conditions, the transmitter, if rated at 75 watts allowable dissipation, would overheat somewhat. The key-down input should therefore be reduced to 75/80 of 400 watts or 375 watts on c.w. as compared to 400 watts p.e.p. on s.s.b.

Much discussion over power measurement is heard on the air, and much of it is confusing. The term "d.c. input" is often used in connection with s.s.b. equipment. Without definition or qualification this term means little or nothing. When one talks into a microphone connected to a s.s.b. transmitter with a typical linear amplifier, the amplifier plate-current meter fluctuates from its resting value to peak values which are much higher. How high these peaks actually go depends on the voice waveform; what we read on the plate meter depends on the meter characteristics. It is often assumed that the highest meter reading is one half of the actual peak value, but this could be in error by a large factor. Actually an oscilloscope in the transmitter output circuit is the only accurate method of measuring peak power. A well set up two-tone measuring system as described in the A.R.R.L. Handbook is another method.

To summarize, both p.e.p. and average power values of input should be measured and understood in order to assure that the station transmitter is operating properly and within legal limits. Normally the s.s.b. peak power rating is the largest, with the c.w. rating close behind, and the a.m. carrier rating only about 25% of the s.s.b. p.e.p. rating.

SUPPORT PROJECT AUSTRALIS!

THE POPULAR

GREAT CIRCLE BEARING MAPS

60c Post Free

Printed on heavy paper 20" x 30", Great Circle Map 16" diameter. Invaluable for all DXers and S.w.'s. Bearings around circumference allow precise beam headings to be made.

ALL PROCEEDS TO W.I.A. PROJECT AUSTRALIS

Cheques, etc., to W.I.A., P.O. Box 67, East Melbourne, Vic., 3002

We would again wish to thank all those people who have bought Maps and who made donations over and above the advertised price.

* Reprinted from "QST," January 1971.

PRACTICAL V.H.F. AND U.H.F. COIL-WINDING DATA*

Complete Details on Inductors from 2 Nanohenries to 1 Microhenry

DONALD KOCHEN, K3SVC

This article contains computer generated data for building inductors from 2 to 1,000 nanohenries (1 nanohenry equals 0.001 μ H.). Since no calculations are involved, it is a simple matter to scan the tables and select the inductor that best meets your particular requirements. The first part of the article describes single-layer solenoids from 10 to 1,000 nH.; the last part describes straight-wire inductors above a chassis that range from 2 to 100 nH.

V.H.F. INDUCTORS

Many v.h.f. experimenters have developed a sixth sense for winding r.f. coils—they've had to, since there does not seem to be any convenient coil winding data for this part of the spectrum. (The A.R.R.L. Lightning Calculator stops at 1 μ H. and the Allied Coil Winding Calculator stops at 0.1 μ H.)

The typical design procedure is to wrap some wire around a pencil (a coil form is also permitted) and trim the coil to resonance with the aid of a grid-dip meter and fixed capacitor. However, it takes a fair amount of experience to select the proper wire size and coil diameter that will give the desired inductance and still have reasonable Q and low capacitance.

Tables 1, 2, 3 and 4 describe coils of 1 to 10 turns wound with an inside diameter of $\frac{1}{8}$ " to $\frac{1}{2}$ ".† Because of their size, these coils are especially attractive for use with solid-state receivers and transmitters.

DESIGN PHILOSOPHY

The goal is an inductor that has high Q, low capacitance and compact size. Low coil capacitance means the inductor will have a high self-resonant frequency, and therefore a more useful frequency range. This can be achieved by a single-layer solenoid with adequate turns spacing. A good rule of thumb is to have a space equal to the wire diameter between adjacent turns with coil length about 1.5 times the coil diameter. The result is a coil with low capacitance and reasonable Q. All coils computed in the tables have turns spacing equal to the diameter of the wire used; as a check, the overall length of the coil is also given.

Those coils whose length is 1 to 2 times diameter are shown in bold type since they are considered to be

optimum. By scanning the tables you can see that any inductance can be obtained by an optimum coil.

All calculated inductances were rounded off to the nearest 10 nanohenries. This means that the error of values below 30 nH. will be ± 5 nH. This seemed sufficient since adjacent objects will introduce errors into the free-space design anyway. Below 10 nH. it is usually easier to build straight-wire inductors.

USING THE TABLES

The tables are intended for air-core coils whose dimensions are indicated in Fig. 1. Each table describes coils wound with a different inside diameter. Wire size and number of turns are specified along the edge of the chart. The data within the table is inductance in nanohenries (on top) and coil length in inches (below). The use of the inductance tables is best illustrated by several practical examples.

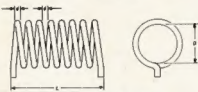


Fig. 1—Air-wound coil showing construction dimensions.

Example 1:

What is the inductance of 5 turns of No. 18 wire, 0.25" diameter, wound with spacing equal to wire diameter?

From Table 2, opposite No. 18, and below 5 turns, you find this coil has 90 nH. inductance and is 0.44" long.

A coil of given inductance can be easily designed by scanning the optimum regions (bold-faced type) of each table. If the exact value is not found, the inductance may be mentally interpolated by changing the turns by a fraction or by compressing or expanding coil length.

Example 2:

A 50 nH. coil is required for a 20-w. transmitter. (Possibility is given first, then a comment.)

0.125" diam., 5 turns No. 24.

Poor choice at this power level.

0.250" diam., 4 turns Nos. 12 or 14.

Fair choice, only slightly out of optimum region.

0.250" diam., $3\frac{1}{2}$ turns No. 16.

Marginal at this power level.

0.250" diam., 3 turns No. 18.

Marginal at this power level.

0.375" diam., 2 $\frac{1}{2}$ turns No. 10.

Good choice.

0.375" diam., 2.7 turns No. 12.

Good choice.

0.375" diam., 2.3 turns No. 14.

Good choice.

0.500" diam., 2 turns No. 10.

Good choice.

0.500" diam., 2 turns No. 12.

Good choice.

Example 3:

Same 50 nH. coil as in Example 2, but this time it is required for a receiver.

0.125" diam., 5 turns No. 24.

Good choice, compact size.

0.250" diam., 3.5 turns No. 16.

Good choice.

0.250" diam., 3 turns No. 18.

Good choice.

0.375" diam., 2.7 turns No. 10.

Good choice, but large size may add too much capacitance to the circuit.

U.H.F. INDUCTORS

As you can see from Tables 1, 2, 3 and 4, it is impractical to wind coils less than 10 nH. For less than 10 nH. the inductance of a straight piece of wire is sufficient. Quarter-wavelength resonators are common in microwave work and may be considered as an inductance in parallel with distributed capacitance.

Full-sized quarter-wave resonators are useful above 1 or 2 GHz. because of their convenient size and high Q. But at 432 MHz. or even 1296, the designer may want a more compact resonator. This can be accomplished by shortening the length needed for quarter-wave resonance and making up for the decreased inductance by adding external capacitance.

Obviously this is a design trade-off resulting in a lower Q, since $Q = X_L/R$, and decreased inductance means lowered Q. However, you have gained more compact size: e.g., 432 MHz. tank circuits may be built 1 or 2 inches long as compared with a full quarter-wavelength of 7 inches. You have also avoided an impedance-matching problem since connecting circuitry will usually be capacitive anyway.

In a transistor tank circuit the collector capacitance, tuning capacitor and coil capacitance are combined. Output is taken by either capacitor-divider coupling, transformer coupling or tapping down on the coil. (Motorola has an excellent application note for r.f. transistor design.)

(Continued on Page 9)

* Reprinted from "Ham Radio," April 1971.

† The tables were computed from the formula

$$L = \frac{(ND)^2}{4.5D + 101} \quad (1)$$

where L is inductance, D is coil diameter and 1 is coil length. This formula approximates the low-frequency inductance of a coil in free space. However, after building a few coils and measuring their inductance with a Boonton 250A RX meter at 100 MHz. it appears that the error is only 10% for most coils.

‡ Instead of winding fractional turns, the coil may be wound with 3 turns and "stretched" to the desired inductance.

| | | |
|--------|--------|--------|
| "OST" | yearly | "CQ" |
| \$8.40 | | \$5.70 |

and others

Through Federal Executive at
Box 67, East Melbourne, 3002

| Wire Size | Number of Turns | | | | | | | | | | |
|-----------|-----------------|------|------|------|------|------|------|------|------|----------|--|
| | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | |
| 18 | 8 | 10 | 20 | 30 | 40 | 50 | 60 | 70 | 80 | nH, InCh | |
| | 0.12 | 0.20 | 0.28 | 0.36 | 0.44 | 0.52 | 0.60 | 0.68 | 0.76 | 0.85 | |
| 20 | 5 | 10 | 20 | 30 | 40 | 50 | 60 | 70 | 80 | nH, InCh | |
| | 0.10 | 0.16 | 0.22 | 0.29 | 0.35 | 0.42 | 0.48 | 0.54 | 0.61 | 0.67 | |
| 22 | 5 | 10 | 20 | 30 | 40 | 50 | 60 | 70 | 80 | nH, InCh | |
| | 0.08 | 0.13 | 0.18 | 0.23 | 0.28 | 0.33 | 0.38 | 0.43 | 0.48 | 0.53 | |
| 24 | 5 | 10 | 20 | 30 | 40 | 50 | 60 | 70 | 80 | nH, InCh | |
| | 0.06 | 0.10 | 0.14 | 0.18 | 0.22 | 0.26 | 0.30 | 0.34 | 0.38 | 0.42 | |

TABLE 1.—Coil data for 0.125 inch diameter air-wound coils.
(Bold-face values represent optimum designs)

| Wire Size | Number of Turns | | | | | | | | | | |
|-----------|-----------------|------|------|------|------|------|------|------|------|----------|--|
| | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | |
| 12 | 10 | 30 | 50 | 70 | 80 | 100 | 120 | 130 | 150 | nH, InCh | |
| | 0.24 | 0.40 | 0.57 | 0.73 | 0.89 | 1.05 | 1.21 | 1.37 | 1.54 | 1.7 | |
| 14 | 10 | 30 | 40 | 50 | 70 | 90 | 110 | 130 | 150 | nH, InCh | |
| | 0.19 | 0.32 | 0.45 | 0.56 | 0.71 | 0.83 | 0.96 | 1.09 | 1.22 | 1.35 | |
| 16 | 10 | 20 | 40 | 60 | 80 | 100 | 120 | 140 | 170 | nH, InCh | |
| | 0.15 | 0.25 | 0.36 | 0.48 | 0.58 | 0.68 | 0.78 | 0.88 | 0.97 | 1.07 | |
| 18 | 10 | 30 | 50 | 70 | 90 | 120 | 140 | 170 | 220 | nH, InCh | |
| | 0.12 | 0.20 | 0.28 | 0.36 | 0.44 | 0.52 | 0.60 | 0.69 | 0.77 | 0.85 | |
| 20 | 10 | 30 | 50 | 70 | 90 | 120 | 150 | 180 | 220 | nH, InCh | |
| | 0.10 | 0.16 | 0.22 | 0.29 | 0.35 | 0.42 | 0.48 | 0.54 | 0.61 | 0.67 | |
| 22 | 10 | 30 | 50 | 70 | 90 | 120 | 150 | 180 | 220 | nH, InCh | |
| | 0.08 | 0.13 | 0.18 | 0.23 | 0.28 | 0.33 | 0.38 | 0.43 | 0.48 | 0.53 | |
| 24 | 10 | 30 | 50 | 70 | 90 | 120 | 150 | 180 | 220 | nH, InCh | |
| | 0.06 | 0.10 | 0.14 | 0.18 | 0.22 | 0.26 | 0.30 | 0.34 | 0.38 | 0.42 | |

TABLE 2.—Coil data for 0.25 inch diameter air-wound coils.
(Bold-face values represent optimum designs)

| Wire Size | Number of Turns | | | | | | | | | | |
|-----------|-----------------|------|------|------|------|------|------|------|------|------|----------|
| | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | |
| 10 | 10 | 30 | 50 | 80 | 110 | 132 | 153 | 170 | 210 | 240 | nH, InCh |
| | 0.31 | 0.51 | 0.71 | 0.92 | 1.12 | 1.32 | 1.53 | 1.73 | 1.94 | 2.14 | |
| 12 | 10 | 30 | 50 | 80 | 120 | 150 | 180 | 210 | 240 | 270 | nH, InCh |
| | 0.24 | 0.40 | 0.57 | 0.73 | 0.89 | 1.05 | 1.21 | 1.37 | 1.54 | 1.70 | |
| 14 | 10 | 30 | 50 | 80 | 120 | 150 | 180 | 210 | 240 | 270 | nH, InCh |
| | 0.19 | 0.32 | 0.45 | 0.58 | 0.71 | 0.83 | 0.96 | 1.09 | 1.22 | 1.35 | |
| 16 | 10 | 30 | 50 | 80 | 120 | 150 | 180 | 210 | 240 | 270 | nH, InCh |
| | 0.15 | 0.25 | 0.36 | 0.48 | 0.58 | 0.68 | 0.78 | 0.88 | 0.97 | 1.07 | |
| 18 | 10 | 30 | 50 | 80 | 120 | 150 | 180 | 210 | 240 | 270 | nH, InCh |
| | 0.12 | 0.20 | 0.28 | 0.36 | 0.44 | 0.52 | 0.60 | 0.69 | 0.77 | 0.85 | |
| 20 | 10 | 30 | 50 | 80 | 120 | 150 | 180 | 210 | 240 | 270 | nH, InCh |
| | 0.10 | 0.16 | 0.22 | 0.29 | 0.35 | 0.42 | 0.48 | 0.54 | 0.61 | 0.67 | |
| 22 | 10 | 30 | 50 | 80 | 120 | 150 | 180 | 210 | 240 | 270 | nH, InCh |
| | 0.08 | 0.13 | 0.18 | 0.23 | 0.28 | 0.33 | 0.38 | 0.43 | 0.48 | 0.53 | |
| 24 | 10 | 30 | 50 | 80 | 120 | 150 | 180 | 210 | 240 | 270 | nH, InCh |
| | 0.06 | 0.10 | 0.14 | 0.18 | 0.22 | 0.26 | 0.30 | 0.34 | 0.38 | 0.42 | |

TABLE 3.—Coil data for 0.375 inch diameter air-wound coils.
(Bold-face values represent optimum designs)

| Wire Size | Number of Turns | | | | | | | | | | |
|-----------|-----------------|------|------|------|------|------|------|------|------|------|----------|
| | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | |
| 12 | 10 | 30 | 50 | 80 | 120 | 150 | 200 | 250 | 300 | 360 | nH, InCh |
| | 0.31 | 0.51 | 0.71 | 0.92 | 1.12 | 1.32 | 1.53 | 1.73 | 1.94 | 2.14 | |
| 14 | 10 | 30 | 50 | 80 | 120 | 150 | 200 | 250 | 300 | 360 | nH, InCh |
| | 0.24 | 0.40 | 0.57 | 0.73 | 0.89 | 1.05 | 1.21 | 1.37 | 1.54 | 1.70 | |
| 16 | 10 | 30 | 50 | 80 | 120 | 150 | 200 | 250 | 300 | 360 | nH, InCh |
| | 0.19 | 0.32 | 0.45 | 0.58 | 0.71 | 0.83 | 0.96 | 1.09 | 1.22 | 1.35 | |
| 18 | 10 | 30 | 50 | 80 | 120 | 150 | 200 | 250 | 300 | 360 | nH, InCh |
| | 0.15 | 0.25 | 0.36 | 0.48 | 0.58 | 0.68 | 0.78 | 0.88 | 0.97 | 1.07 | |
| 20 | 10 | 30 | 50 | 80 | 120 | 150 | 200 | 250 | 300 | 360 | nH, InCh |
| | 0.12 | 0.20 | 0.28 | 0.36 | 0.44 | 0.52 | 0.60 | 0.69 | 0.77 | 0.85 | |
| 22 | 10 | 30 | 50 | 80 | 120 | 150 | 200 | 250 | 300 | 360 | nH, InCh |
| | 0.10 | 0.16 | 0.22 | 0.29 | 0.35 | 0.42 | 0.48 | 0.54 | 0.61 | 0.67 | |
| 24 | 10 | 30 | 50 | 80 | 120 | 150 | 200 | 250 | 300 | 360 | nH, InCh |
| | 0.08 | 0.13 | 0.18 | 0.23 | 0.28 | 0.33 | 0.38 | 0.43 | 0.48 | 0.53 | |
| 26 | 10 | 30 | 50 | 80 | 120 | 150 | 200 | 250 | 300 | 360 | nH, InCh |
| | 0.06 | 0.10 | 0.14 | 0.18 | 0.22 | 0.26 | 0.30 | 0.34 | 0.38 | 0.42 | |

TABLE 4.—Coil data for 0.5 inch diameter air-wound coils.
(Bold-face values represent optimum designs)

| Wire Size | Length (Inches) | | | | | | | | | | |
|-----------|-----------------|-----|-----|-----|-----|-----|-----|-----|-----|-----|----------|
| | 0.5 | 1.0 | 1.5 | 2.0 | 2.5 | 3.0 | 3.5 | 4.0 | 4.5 | 5.0 | |
| 2 | 2 | 5 | 8 | 9 | 12 | 15 | 16 | 22 | 26 | 29 | 32 |
| | 0.2 | 0.4 | 0.7 | 1.1 | 1.5 | 1.8 | 2.2 | 2.5 | 2.9 | 3.3 | 3.6 |
| 4 | 3 | 6 | 10 | 14 | 16 | 22 | 26 | 30 | 34 | 38 | nH, InCh |
| | 0.3 | 0.6 | 0.8 | 1.1 | 1.4 | 1.7 | 2.0 | 2.3 | 2.6 | 2.8 | |
| 6 | 3 | 7 | 12 | 17 | 21 | 25 | 30 | 35 | 40 | 44 | nH, InCh |
| | 0.3 | 0.5 | 0.7 | 0.9 | 1.2 | 1.5 | 1.8 | 2.1 | 2.4 | 2.7 | |
| 8 | 3 | 5 | 2.5 | 1.6 | 1.2 | 0.9 | 0.7 | 0.6 | 0.5 | 0.5 | nH, InCh |
| | 0.2 | 0.4 | 0.6 | 0.8 | 1.0 | 1.2 | 1.4 | 1.6 | 1.8 | 2.0 | |
| 10 | 3 | 5 | 2.5 | 1.6 | 1.2 | 0.9 | 0.7 | 0.6 | 0.5 | 0.5 | nH, InCh |
| | 0.2 | 0.4 | 0.6 | 0.8 | 1.0 | 1.2 | 1.4 | 1.6 | 1.8 | 2.0 | |
| 12 | 3 | 5 | 2.5 | 1.6 | 1.2 | 0.9 | 0.7 | 0.6 | 0.5 | 0.5 | nH, InCh |
| | 0.2 | 0.3 | 0.5 | 0.8 | 0.9 | 0.9 | 1.1 | 1.3 | 1.4 | 1.6 | |
| 14 | 3 | 5 | 2.5 | 1.6 | 1.2 | 0.9 | 0.7 | 0.6 | 0.5 | 0.5 | nH, InCh |
| | 0.2 | 0.3 | 0.5 | 0.8 | 0.9 | 0.9 | 1.1 | 1.3 | 1.4 | 1.6 | |
| 16 | 3 | 5 | 2.5 | 1.6 | 1.2 | 0.9 | 0.7 | 0.6 | 0.5 | 0.5 | nH, InCh |
| | 0.2 | 0.3 | 0.5 | 0.8 | 0.9 | 0.9 | 1.1 | 1.3 | 1.4 | 1.6 | |
| 18 | 3 | 5 | 2.5 | 1.6 | 1.2 | 0.9 | 0.7 | 0.6 | 0.5 | 0.5 | nH, InCh |
| | 0.2 | 0.3 | 0.5 | 0.8 | 0.9 | 0.9 | 1.1 | 1.3 | 1.4 | 1.6 | |
| 20 | 3 | 5 | 2.5 | 1.6 | 1.2 | 0.9 | 0.7 | 0.6 | 0.5 | 0.5 | nH, InCh |
| | 0.2 | 0.3 | 0.5 | 0.8 | 0.9 | 0.9 | 1.1 | 1.3 | 1.4 | 1.6 | |
| 22 | 3 | 5 | 2.5 | 1.6 | 1.2 | 0.9 | 0.7 | 0.6 | 0.5 | 0.5 | nH, InCh |
| | 0.2 | 0.3 | 0.5 | 0.8 | 0.9 | 0.9 | 1.1 | 1.3 | 1.4 | 1.6 | |
| 24 | 3 | 5 | 2.5 | 1.6 | 1.2 | 0.9 | 0.7 | 0.6 | 0.5 | 0.5 | nH, InCh |
| | 0.2 | 0.3 | 0.5 | 0.8 | 0.9 | 0.9 | 1.1 | 1.3 | 1.4 | 1.6 | |

TABLE 5.—Inductance of wire 0.25 inch above a ground plane.
(Upper value is inductance in nH, middle value is capacitance in pF, lower value is self-resonant frequency in GHz.)

| Wire Size | Length (Inches) | | | | | | | | | | |
|-----------|-----------------|-----|-----|-----|-----|-----|-----|-----|-----|-----|-------------|
| | 0.5 | 1.0 | 1.5 | 2.0 | 2.5 | 3.0 | 3.5 | 4.0 | 4.5 | 5.0 | |
| 2 | 0.2 | 0.4 | 0.6 | 0.8 | 1.0 | 1.2 | 1.4 | 1.6 | 1.8 | 2.0 | nH, pF, GHz |
| | 9.3 | 2.7 | 1.7 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | |
| 4 | 3 | 8 | 14 | 19 | 25 | 31 | 38 | 42 | 48 | 54 | nH, pF, GHz |
| | 6.2 | 2.7 | 1.7 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | |
| 6 | 4 | 9 | 15 | 21 | 28 | 34 | 40 | 47 | 53 | 59 | nH, pF, GHz |
| | 6.2 | 2.7 | 1.7 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | |
| 8 | 4 | 9 | 15 | 21 | 28 | 34 | 40 | 47 | 53 | 59 | nH, pF, GHz |
| | 6.2 | 2.7 | 1.7 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | |
| 10 | 4 | 9 | 15 | 21 | 28 | 34 | 40 | 47 | 53 | 59 | nH, pF, GHz |
| | 6.2 | 2.7 | 1.7 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | |
| 12 | 5 | 13 | 20 | 28 | 36 | 44 | 53 | 61 | 69 | 77 | nH, pF, GHz |
| | 5.8 | 2.7 | 1.7 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | |
| 14 | 6 | 14 | 22 | 31 | 39 | 48 | 57 | 65 | 74 | 83 | nH, pF, GHz |
| | 5.8 | 2.7 | 1.7 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | |
| 16 | 6 | 14 | 22 | 31 | 39 | 48 | 57 | 65 | 74 | 83 | nH, pF, GHz |
| | 5.8 | 2.7 | 1.7 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | |
| 18 | 7 | 16 | 26 | 35 | 45 | 55 | 65 | 75 | 85 | 94 | nH, pF, GHz |
| | 5.8 | 2.6 | 1.7 | 1.2 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | |
| 20 | 7 | 17 | 27 | 36 | 46 | 56 | 66 | 76 | 86 | 96 | nH, pF, GHz |
| | 5.8 | 2.6 | 1.7 | 1.2 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | |
| 22 | 8 | 18 | 28 | 37 | 47 | 57 | 67 | 77 | 87 | 97 | nH, pF, GHz |
| | 5.5 | 2.6 | 1.7 | 1.2 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | |
| 24 | 9 | 19 | 31 | 42 | 54 | 65 | 77 | 89 | 100 | 112 | nH, pF, GHz |
| | 5.5 | 2.6 | 1.7 | 1.2 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | |

TABLE 6.—Inductance of wire 0.5 inch above a ground plane.
(Upper value is inductance in nH, middle value is capacitance in pF, lower value is self-resonant frequency in GHz.)

Tables 5, 6 and 7 contain computed data describing a wire of diameter D and length L , spaced height H above a ground plane as shown in Fig. 2. Wire size, height above ground and length in inches are specified along the edges of the inductance tables. The data within the table is inductance (nH), on top, capacitance (pF), in the middle, self-resonance (GHz), on the bottom. As before, the use of these tables is best illustrated by several typical examples.

Example 4:

What are the characteristics of a 2" length of No. 10 wire, spaced 0.25" above a ground plane?

From Table 5, a 2" length of No. 10 wire has 21 nH inductance in parallel with 0.7 pF. Self-resonant frequency 1.2 GHz. (1200 MHz.)

DESIGN PHILOSOPHY

A quick scan of Tables 5, 6 and 7 reveals some interesting phenomena that should be kept in mind when laying out circuits. For example, moving the inductor closer to a ground plane increases its capacitance. Not so obvious is the fact that this also decreases inductance. The inductor and the ground plane may be considered



Fig. 2—Length of wire above a ground plane exhibits both inductance and capacitance. Dimensions are used to calculate values.

The inductance values shown in Tables 5, 6 and 7 were calculated from the formula

$$L = .0116967 (\log 4H/D + \log \frac{A}{8}) + .00508 (B-A + \mu \log \frac{A}{8} - 2H + \frac{D}{2})$$

$$\text{where } A = 1 + \sqrt{1 + \frac{D^2}{4}}$$

$$B = 1 + \sqrt{1 + 4H^2}$$

$$\mu (\text{permeability}) = 1$$

Skin effect, because of its very small value, was neglected. The capacitance of the straight wire above a ground plane was calculated from

$$C = \frac{\pi \epsilon l}{\ln(4H/D)}$$

where ϵ is permittivity. As a check, capacitance measurements were made on a Bonton 80A RLC meter operating at 1 GHz. Readings were within 0.4 pF of the calculated values. Next, the circuit of Fig. 2 was duplicated, and a signal generator and rf detector were loosely coupled to the resonator. For each coil measured the self-resonant frequency was within 20% of that calculated from the computed inductance and capacitance. It is also gratifying that there is some correlation between the computed LC resonant frequency and resonance of quarter-wave transmission lines.

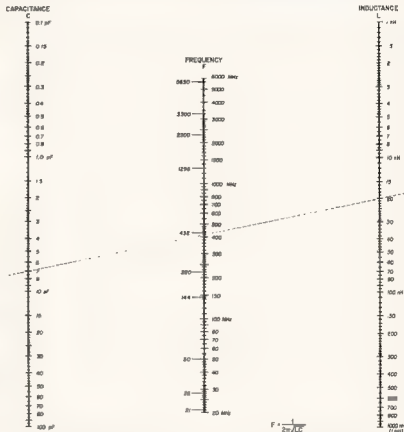


Fig. 4—Resonant-frequency nomogram may be used to determine capacitor and inductor values over range from 20 to 8,000 MHz. The example indicates that 20 nH will resonate at 425 MHz, with a 7 pF capacitor.

| Wire Size | Length (Inches) | | | | | | | | | | Wire Size | Length (Inches) | | | | | | | | | | | | | |
|-----------|-----------------|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----------|-----------------|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|------|
| | 0.5 | 1.0 | 1.5 | 2.0 | 2.5 | 3.0 | 3.5 | 4.0 | 4.5 | 5.0 | | 0.5 | 1.0 | 1.5 | 2.0 | 2.5 | 3.0 | 3.5 | 4.0 | 4.5 | 5.0 | | | | |
| 2 | 3 | 8 | 14 | 21 | 27 | 34 | 41 | 47 | 54 | 61 | nH. | 14 | 6 | 18 | 24 | 34 | 44 | 55 | 65 | 75 | 85 | 98 | nH. | | |
| | 0.1 | 0.3 | 0.4 | 0.5 | 0.7 | 0.9 | 1.0 | 1.1 | 1.3 | 1.4 | pF. | | 16 | 0.1 | 0.2 | 0.3 | 0.4 | 0.5 | 0.6 | 0.7 | 0.7 | 0.8 | 0.9 | pF. | |
| | 1.1 | 3.0 | 1.9 | 1.3 | 1.0 | 0.9 | 0.7 | 0.6 | 0.5 | 0.5 | GHz. | | | 18 | 6.2 | 2.8 | 1.8 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | GHz. |
| 4 | 3 | 9 | 16 | 23 | 30 | 37 | 45 | 52 | 59 | 67 | nH. | 16 | | | 7 | 10 | 26 | 37 | 47 | 58 | 68 | 80 | 91 | 102 | nH. |
| | 0.1 | 0.3 | 0.4 | 0.5 | 0.7 | 0.9 | 0.9 | 1.1 | 1.2 | 1.3 | pF. | | 18 | | 0.1 | 0.2 | 0.3 | 0.4 | 0.4 | 0.5 | 0.6 | 0.7 | 0.8 | 0.9 | pF. |
| | 0.9 | 3.0 | 1.8 | 1.3 | 1.0 | 0.9 | 0.7 | 0.6 | 0.5 | 0.5 | GHz. | | | 20 | 8.1 | 2.8 | 1.8 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | GHz. |
| 6 | 4 | 10 | 18 | 25 | 33 | 41 | 49 | 57 | 65 | 73 | nH. | 18 | | | 7 | 17 | 28 | 39 | 50 | 62 | 73 | 85 | 96 | 108 | nH. |
| | 0.1 | 0.2 | 0.4 | 0.5 | 0.6 | 0.7 | 0.8 | 1.0 | 1.1 | 1.2 | pF. | | 20 | | 0.1 | 0.2 | 0.3 | 0.3 | 0.4 | 0.5 | 0.5 | 0.6 | 0.7 | 0.8 | pF. |
| | 0.7 | 2.9 | 1.8 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | GHz. | | | 22 | 5.8 | 2.7 | 1.7 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | GHz. |
| 8 | 5 | 11 | 19 | 27 | 36 | 44 | 53 | 61 | 70 | 79 | nH. | 20 | | | 8 | 18 | 30 | 41 | 53 | 65 | 77 | 89 | 101 | 114 | nH. |
| | 0.1 | 0.2 | 0.3 | 0.5 | 0.6 | 0.7 | 0.8 | 0.9 | 1.0 | 1.1 | pF. | | 22 | | 0.1 | 0.2 | 0.2 | 0.3 | 0.4 | 0.5 | 0.5 | 0.6 | 0.7 | 0.8 | pF. |
| | 0.5 | 2.8 | 1.8 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | GHz. | | | 24 | 5.8 | 2.7 | 1.7 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | GHz. |
| 10 | 5 | 12 | 21 | 30 | 39 | 48 | 57 | 66 | 75 | 84 | nH. | 22 | | | 8 | 19 | 31 | 44 | 56 | 69 | 81 | 94 | 107 | 119 | nH. |
| | 0.1 | 0.2 | 0.3 | 0.4 | 0.5 | 0.6 | 0.7 | 0.8 | 0.9 | 1.1 | pF. | | 24 | | 0.1 | 0.2 | 0.2 | 0.3 | 0.4 | 0.5 | 0.5 | 0.6 | 0.7 | 0.8 | pF. |
| | 0.4 | 2.8 | 1.8 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | GHz. | | | 26 | 5.8 | 2.7 | 1.7 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | GHz. |
| 12 | 5 | 14 | 23 | 32 | 41 | 51 | 61 | 71 | 80 | 90 | nH. | 24 | | | 9 | 21 | 33 | 46 | 59 | 72 | 85 | 99 | 112 | 125 | nH. |
| | 0.1 | 0.2 | 0.3 | 0.4 | 0.5 | 0.6 | 0.7 | 0.8 | 0.9 | 1.0 | pF. | | 26 | | 0.1 | 0.2 | 0.2 | 0.3 | 0.4 | 0.4 | 0.5 | 0.5 | 0.6 | 0.7 | 0.7 |
| | 0.3 | 2.8 | 1.8 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | GHz. | | | 28 | 5.8 | 2.7 | 1.7 | 1.3 | 1.0 | 0.8 | 0.7 | 0.6 | 0.5 | 0.5 | GHz. |

TABLE 7.—Inductance of wire 1.8 inch above a ground plane.

(Upper value is inductance in nH, middle value is capacitance in pF, lower value is self-resonant frequency in GHz.)

to be a transformer with a shorted secondary. Hence, increased coupling results in less inductance. It turns out that the capacitance changes more than inductance, and the net result is a lower resonant frequency.

Moving the inductor away from the chassis will raise the Q. Beyond a height of one inch, however, the computed L and C rapidly approaches the free-space inductance as a limit, and the law of diminishing returns applies.

Considering the resonator as a transmission line, its characteristic impedance is $Z_0 = \sqrt{L/C}$. Thus, moving the quarter-wave resonator too far from the chassis will raise its impedance to match the approximately 377-ohm radiation resistance of space. Then the resonator will then behave more like an antenna than a resonator.

Adding additional ground planes at right angles to form co-axial cavity around the wire lowers the resonant frequency by about 10%. This implies that L and C have changed by more than that amount since they move in opposite directions. An estimate of the inductance and capacitance of a co-axial shielded wire can be made by considering it simply as a wire that is closer to a single ground plane.

U.h.f. resonators are usually made from the larger diameter wires, but data for wires smaller than No. 18 is included mainly for estimating component lead inductance. The resonant frequency given in the table sets the upper limit at which the inductor may be used; above resonance it acts like a capacitor. The inductor should be chosen so that with the added external circuit capacitance the LC combination will resonate at the desired frequency.

SUMMARY

It is one thing to design on paper but u.h.f. and microwave work always require a certain amount of "cut and try". The approximations made and factors ignored in this article would probably send chills up the spine of a physicist. However, physicists don't have to design equipment and make things work.

Each piece of equipment is a unique problem. Armed with basic data and some mental fudge factors, the designer can obtain a quick solution of reasonable accuracy. Compared to that, an exact calculation is usually impractical.

REFERENCES

- 1 "Reference Data for Radio Engineers," fifth edition, I.T.T.
- 2 Frank Davis, "Matching Network Designs with Computer Solutions," Motorola Application Note AN-287, Motorola Semiconductor Products, Inc., Box 990, Phoenix, Arizona.
- 3 Keith Henney, Radio Engineering Handbook, McGraw-Hill, New York.
- 4 John Ryder, "Network Lines and Fields," 2nd edition, 1948, Prentice-Hall, New York.

Book Review

UNDERSTANDING AMATEUR RADIO

Publisher: A.E.R.L. Cover price \$US2.50

Amateur Radio has something to interest all types of people. Amateur Radio also provides a training ground wherein newcomers can learn Electronics and Communications principles and practices. "Understanding Amateur Radio" takes the newcomer through from first principles to a complete and quite elaborate station in a clear and concise manner. See the Secretary of your Division for this and many other interesting titles, or write to Federal Executive.—VK3ASC.

ANGLE MODULATION

(Continued from Page 5)

condenser, connected across the oscillator tuned circuit and this brings the oscillator back on its centre frequency if it drifts.

In another method the two-phase motor is replaced with an automatic frequency control (a.f.c.) which produces a voltage whose polarity depends on the direction of the oscillator drift and the amplitude is governed by the amount of drift. This voltage is applied as bias to the grid of the reactance valve modulator or to the varactors if they are being used to derive the frequency modulation.

As has been stated, it is difficult to frequency modulate a quartz crystal, but the Marconi Co. developed a method using a quarter wave transmission line between a reactance valve modulator and a quartz crystal. The crystal oscillates at 1/24th of the carrier frequency and the reactance valve modulator is capable of swinging the crystal frequency ± 3.125 KHz. When the crystal frequency is multiplied twenty-four times to obtain the carrier frequency the deviation is ± 75 KHz. There is i.m. sound broadcasting in Britain and ± 75 KHz. is the maximum deviation permitted.

(to be continued)

ERRATUM

Re article "Angle Modulation," Lecture No. 14A, in July 1971 "A.R.," page 9, column 1, second complete paragraph: The cut-off frequency should read 74 KHz., not 14 KHz.

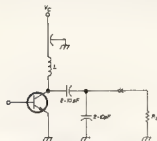


Fig. 3—Typical 425 MHz. tank circuit. Effective circuit capacitance of 7.4 pF will resonate with 19 nH at 424 MHz.

Example 5:

It is desired to design a transistor tank circuit for 430 MHz. as shown in Fig. 3. The transistor has an output capacitance of 3 pF., and the two impedance-matching variable capacitors are assumed to present an average capacitance of 4 pF. at the collector. Thus, total capacitance will be 7 pF. plus inductor capacitance. An LC nomograph (Fig. 4) indicates that 20 nH. will resonate with 7 pF. at 425 MHz.

The data for No. 14 wire spaced 0.25" above a ground plane (Table 5) shows that a 14" length has 17 nH. inductance and 10.5 pF. capacitance. Therefore, the tank circuit consists of 19 nH. in parallel with 17.4 pF. and has a mid-range resonance of 424 MHz.

BRIGHT STAR CRYSTALS

FOR ACCURACY, STABILITY, ACTIVITY
AND OUTPUT

SPECIAL OFFER—

STANDARD AMATEUR CRYSTALS

STYLE HC8U HOLDER, FREQUENCY RANGE 6 TO 15 MHz.

0.01% \$4.25

0.005% \$5.50

Prices include Sales Tax and Postage

COMMERCIAL CRYSTALS

IN HC8U HOLDER, 0.005% TOLERANCE, FREQUENCY RANGE 6 TO 15 MHz.

\$6.00 plus Sales Tax and Postage

Write for list of other tolerances and frequencies available.

COMPREHENSIVE PRICE LIST NOW AVAILABLE—WRITE FOR YOUR COPY

New Zealand Representatives: Messrs. Carroll & Carroll, Box 2102, Auckland

Contractors to Federal and State Government Departments

BRIGHT STAR CRYSTALS PTY. LTD.

LOT 6, EILEEN ROAD, CLAYTON, VIC., 3168

Phone 546-5076

With the co-operation of our overseas associates our crystal manufacturing methods are the latest

V.H.F. METEOR SCATTER PROPAGATION

Hints on using Meteor Trail Ionisation for Six Metre DX

WALLY WATKINS,* VK5ZWW (ZL2TCW)

In most textbooks towards the end of the chapter dealing with v.h.f. propagation, reference is made to the esoteric forms of communication. However one look at the table, which shows antenna power and receiver capabilities necessary for these forms, usually puts paid to any idea of using them.

Meteor scatter is no mode for the casual operator. However, it is within the grasp of all v.h.f. operators in Australia who have reasonable gear, ample patience and operating skill at both ends of the path.

Since August 1970 experiments and tests have been carried out to determine power levels and antennae required for meteor scatter in Australia. The path Tennant Creek, N.H., and Adelaide, S.A., was used for primary evaluation, the distance being 1,100 miles. Antennae and receiving set-up was similar at each end of the path but transmitter power was different.

As is generally known, the meteor signal is reflected, not from the particle itself, usually the size of a grain of sand, but from the stream of ionisation left by the meteor as it is heated and vaporised by friction with the atmosphere.¹ This takes place in the E layer, about 100 km. above the earth, so that distances worked closely correspond with those of E_s propagation.

It must be pointed out at this stage that there are two sets of conditions existing for meteor scatter propagation. Firstly random meteors exist throughout the twenty-four hours peaking to a maximum at 0800 local sun time and dropping to a minimum at 1800 hours. The second is when the earth passes through a belt of space debris, which is predictable from year to year, and is known as a meteor shower. For those who wish to delve more deeply into the mechanics of meteor scatter, the classic article by Walt W4LTU in "QST" of April 1957 is recommended.

It has been found that the minimum transmit requirements are well within the scope of the average Amateur. A 6 element beam is quite satisfactory provided it is up high enough to clear surrounding objects. The transmitter should run a 6/40 in the final with either 800 or 1,000 volts on the anodes. It is assumed that one is running s.b. and the 6/40 is operating in AB1.

At this location the FT-DX-100 runs into a homebrew transverter using an 880CF oscillator-buffer at 24 MHz, a 6939 mixer-driver and a 6/40 with 1,000 volts on the anodes. The converter is a VK3 FET with oscillator injection from the 880CF. The antenna is a 9 element yagi on a 30-foot boom.

Because it is possible to talk faster than the average Amateur can copy

c.w., s.b. is superior for this type of propagation. A voice average is about 80 w.p.m. and even though only bits of words are heard at a time, the whole text can be more easily pieced together. It is not intended to denigrate c.w., for c.w. has been found to be a convenient way of station identification, especially with solid state programmed keyers. However s.b. is usually used for the actual exchange of reports.

WHAT IS NEEDED?

What is now needed to make an actual contact via meteor scatter? First you must arrange for someone to be on frequency at the appropriate time. Thereafter patience is needed. It is here that the phrase "esoteric communication" takes on real meaning. If one participant has had previous experience and has passed on this experience to the other, then everything will fall readily into place.

For random meteors a five-minute calling period is used with each station taking alternate turns to call and listen. The identification, call signs and/or reports are repeated for the five-minute period. I have found that pre-recorded endless tapes are ideal for this purpose. During the peak of a known shower, the technique changes. The five-minute calling periods are retained, however station identification is given followed by a key-up period of three seconds. This allows for a form of break-in operation and enables the other station to attempt a reply on the same meteor trail. The second method can be used during random meteor attempts but it is not recommended until some experience is obtained using the first method.

Frequency readout should be capable of an accuracy of ± 500 Hz, and timing of segments can be synchronised with VNG or WWV. Over most paths enough is received during the first five-minute segment to v.f.o. onto the frequency and this is desirable even though it may be slightly off the nominal frequency.

What frequency should be used? This is a matter of personal choice and would be one subject brought up when arranging skeds. Two stations at one end of the path would be advised not to transmit during the same five-minute segment as this would preclude break-in operation. It is also recommended that stations calling with an easterly component in their antenna heading should call during the odd five-minute segments of the hour and those with

a westerly component listen during the odd five-minute segments. During the even segments the roles are reversed.

Identification in the form "This is VK5AA" is acceptable, but phonetics must not be used. Identification is kept up until something definite is heard, then a special reporting system is used or if a contest is on the usual cypher is given.

REPORTING

Reporting coding for s.b. is as follows (c.w. coding would consist of only the initial letter or letters):

Tango (T) = Bits—not enough to identify.

Mexico (M) = Words which can be pieced together to make out call signs and/or report.

Oscar (O) = Both call signs and/or report copied in a single burst.

Roger (R) = Report received.

Combinations of M-R and O-R should be self explanatory and are frequently used. For "break-in" type of operation, providing it has been arranged in advance, there is no need to include the word "break" in the identification as this would be a waste of valuable time. Once contact has been established much time can be saved if extraneous matter in the way of call signs is kept to a minimum. The report or cypher is the important matter to get across and must, of course, be repeated more frequently.

If you are interested in trying this form of propagation you will find it is now up to you to take that first step and arrange that first sked—you will be surprised by how much you hear.

Meteor scatter should lead to some good "Ross Hull" scores this year, especially during the "Geminids" shower in December. On 13th and 14th December, 1970, VK8AU and VK5ZWW swapped two cyphers via M/S using break-in operation, so it can be done.

Thank you to those who have kept skeds with me (between 0500 and 2400), namely VK8AU, VK8KK, VK4RO, VK4ZQ, VK2ZNS, VK2ZRH, VK1PV, VK3ASV, VK3ZQC, VK5ZDX, VK5QZ and VK5ZDY, and to those 6 metre operators in Adelaide who have put up with endless hours of endless tape giving my identification.

REFERENCES

1. "QST," April 1957, p. 28.
2. Up to 30th June, 1971.

* 244 Shepherds Hill Rd., Bellevue Heights, S.A., 5050.



KATSUMI MODEL EK-26 ELECTRONIC KEYS

Features:

- 11 transistors and 12 diodes solid state electronic keys.
- Variable speed key capable of 8 to 60 w.p.m. semi or fully automatic.
- Fully digital dot-dash ratio, always perfect, and speed adjustment.
- Relay or transistor switch output option. (Tr. switch max. 110v, 100 mA.
- Relay max 700v, 500 mA.)
- Built-in break in DSO (VOX-CW) terminal.
- Built-in monitor-oscillator with speaker, and phone jack.
- Power Supply 230v 50-60 Hz AC but 1.5m from ext. batt. two x 9v DC.
- Small in size 140 (w.) x 70 (h.) x 150 (d.) mm. Weight: 3 lb. 12 oz.

Price \$75.00

AUSTRALIAN AGENT:

BAIL ELECTRONIC SERVICES

N.S.W. Rep: STEPHEN KUHIL, P.O. Box 36, Mascot, N.S.W., 2020. Telephone: Day 67-1650 (AH 371-5445)
 South Aust: Rep. FARMERS RADIO PTY. LTD., 257 Angus Street, Adelaide, S.A., 5006. Telephone 23-1288
 Western Aust.: Rep.: N. R. PRIDE, 26 Lockhart Street, Como, W.A., 6132. Telephone 65-4379

CW- PHONE Accessories



KATSUMI MODEL MC-22 MIC. COMPRESSOR

NEW IMPROVED MODEL

Specifications:

Compression level 26 dB (1 KHz) with meter (comp. level variable).
 Output voltage 50 mV max. at input 3 mV.
 Microphone impedance 10-100K ohms, switchable.
 Frequency response 300 5,000 Hz plus or minus 2 dB
 S/N ratio: more than -50 dB
 Transistors used: 3 transistors and 2 diodes
 Power source, consumption: Battery type 216 or D5P (9v), 2 mA max.
 Dimensions 120 (w.) x 70 (h.) x 80 (d.) mm.
 Weight 1 lb 5 oz

Accessories: Jack and plug.

Price \$28.00

Prices and Specifications subject to change.

60 SHANNON STREET, BOX HILL NORTH,
VIC., 3129. Telephone 89-2213

SPECIAL LOW PRICES! (WHILE PRESENT STOCKS LAST) UP-DATE YOUR RECEIVER WITH CFS-455

MODEL CFS-455 is a high class ladder type I.F. filter, which makes use of the piezo-electric effect on lead-zirconate-titanate ceramics and is the modern equivalent of the conventional I.F.T.

This filter is well suited to transistor applications, especially to high quality communications receivers. It has the advantages of high selectivity, low impedance, no alignment, plus miniature size and light weight.

The outer dimensions of Model CFS-455 are as shown at the left. A nickel-brass case is mounted on a plastic base with pins designed for printed circuit mounting.

Specifications of Models now available from stock:—

| Model | Centre Freq (KHz) | 3 dB Bandwidth (KHz.) Min. | 6 dB Bandwidth (KHz.) Min. | 60 dB Bandwidth (KHz.) Max. | 70 dB Bandwidth (KHz.) Max. | Insertion Loss (dB.) Max. | In. Output Impedance (Ω) | Temp Range (°C.) | Discount Price (+27½% S.T. if applicable) |
|-----------|-------------------|----------------------------|----------------------------|-----------------------------|-----------------------------|---------------------------|--------------------------|------------------|---|
| CFS-455 A | 455 | ±13 | ±17.5 | — | ±30 | 6 | 1500 | — | \$12.00 |
| CFS-455 E | 455 | ±5.5 | ±8 | — | ±15 | 8 | 1500 | —20 | \$12.00 |
| CFS-455 G | 455 | — | ±4 | ±9 | — | 8 | 2000 | to | \$16.80 |
| CFS-455 J | 455 | — | ±1.5 | ±4.5 | — | 10 | 2000 | +80 | \$16.80 |

Stability of Centre Frequency: Within 0.4% for 10 years: within ±0.3% from -20°C. to +80°C.

Available from:— **IRH COMPONENTS PTY. LIMITED**
 THE CRESCENT, KINGSGROVE, N.S.W., 2208 — 74 RAGLAN ST., PRESTON, VIC., 3072

HOME STATION ANTENNA FOR 160 METRES

Part Four—Practical Application

J. A. ADCOCK,* M.I.E. (Aust.) VK3ACA

VERTICAL vs. HORIZONTAL FOR TRANSMITTING

As can be seen from Fig. 1, the majority of signal from a vertical is along the ground and zero in the vertical direction, whereas with a horizontal the signal is zero along the ground and maximum vertically. Since surface wave propagation is by the vertically polarised mode only, only the vertical component is useful in surface wave propagation. During the day this mode of propagation may be useful over a distance of 100 miles over flat country—example, Melbourne to Colac, propagation is poor over mountainous country being not much use more than 10 miles. At night propagation via the ionosphere is possible.

With the vertical antenna signals reflected via the ionosphere will be weak close to the transmitter and strong some distance away. This gives rise to a dead zone between the limits of the ground wave and the sky wave. If the lobe signal strength from a horizontal and a vertical were equal, the strength of the rays at 45° to the ground would be equal, this corresponds to a distance of approximately 350 miles. In fact if the vertical and horizontal were of equal efficiency, the peak lobe signal strength at right angles to the wire is greater for the horizontal than the vertical.

Where the horizontal antenna is less efficient (this includes most practical cases for short antennas close to the ground) the area in which the horizontal is advantageous becomes less. A horizontal with an efficiency of only half that of the vertical will still give an advantage over a distance from 300 to 400 miles. The use of a horizontal of very poor efficiency can provide a useful signal in the dead zone (between 20 and 100 miles at night).

The distance over which the horizontal should be preferable to the vertical is shown in the graph Fig. 16. The graph is based on the assumption of an ionosphere height of 180 miles and a flat earth. (Efficiency referred to is power efficiency as calculated by the methods given in other sections.) These assumptions are reasonable for late at night and over the distances considered. If it is desired to apply the graphs to other ionospheric heights the distances can be worked out by simple proportion.

VERTICAL vs. HORIZONTAL FOR RECEIVING

For receiving surface waves the same applies to receiving as transmitting—the receiving antenna must be largely vertical for best results. For receiving signals via the ionosphere, the situation is quite different. Since a signal loses polarisation via the ionosphere it does not follow that the transmitting and receiving antennas must be of the same polarisation. The receiving patterns for the two antennas will be the same as their transmitting patterns.

Since the main concern of a receiver is signal to noise ratio, relative efficiencies of receiving antennas are of no significance (it being assumed that the antenna noise is well above the threshold noise of the receiver). The main consideration is the angle from which the noise is coming. The majority of local noises are vertically polarised. The majority of distant static is received at a low angle and therefore received best on a vertical antenna. Local storms and storms within a radius of 500 miles will probably produce a stronger noise on a horizontal antenna.

Because most noise is received best on a vertical antenna, very considerable advantages can accrue from using a horizontal receiving antenna. Another advantage of a well balanced

horizontal is that it gives good rejection against strong local signals. The best mode of the receiving antenna under different noise conditions for different propagation distances are shown in Table 1.

It can often happen that an interstate or country signal can be almost inaudible on a vertical antenna and 5 and 8 on a horizontal.

To take full advantage of horizontal reception it is desirable that the antenna should have practically no vertical component. This is difficult to achieve because of the tendency of the vertical component to dominate. For best results the virtual ground should be parallel with the antenna. The antenna, feeders and tuning unit should be balanced and as symmetrical as possible. The position is complicated by surrounding buildings. Objects like drain pipes and iron roofs may be sufficiently coupled to the antenna to produce a considerable vertical component and thus destroy some of the properties of the horizontal.

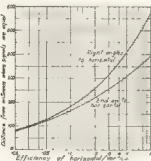


Fig. 16—The distance in miles from the antenna up to which the horizontal is advantageous, is plotted against comparative efficiency. The curves are for signals reflected from an ionosphere 180 miles high by a single hop. The earth is assumed to be flat and the effect is illustrated in Fig. 17.

Antennas of equal efficiency would produce signals of equal signal strength at distances of up to 600 miles broadside to the horizontal or 400 miles end on. Inside these distances from the transmitter the signal from the horizontal would be stronger. Outside these distances the signal from the vertical would usually be stronger. This effect is illustrated in Fig. 17. (These figures are based on the assumption that the signals are mainly reflected by the F layer at night. This is true at least at high angle radiation. The matter is more complicated when considering lower layer reflection.)

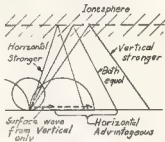


Fig. 17—Illustrating how a horizontal with an efficiency less than that of a vertical can produce a stronger signal in a limited area.

CALCULATIONS AND DISCUSSION

The purpose of this discussion is to examine results obtained in practice and to endeavour to make some useful conclusions. Most of the practical results agree with those obtained by calculations. Some of the conclusions drawn are largely supposition, but should be useful to any person who is experimentally inclined and would like to try them in practice.

The antenna used by the author is a horizontal centre fed length of wire 84 feet long and 30 high. The feeders

| | Low Noise Conditions | High Noise Conditions |
|---|----------------------------------|------------------------------|
| 1. Surface Wave | Vertical | Vertical |
| 2. Intermediate distances up to 800 miles | Horizontal or sometimes Vertical | Horizontal |
| 3. Long distances | Vertical | Either, depending on results |

Table 1.

* P.O. Box 106, Preston, Vic. 3072.

are sloping but these have been considered vertical. The feeders can be fed either in parallel against ground or as a doublet. The normal earth consists of a water pipe driven into the ground close to the transmitter plus four radials at right angles averaging 20 feet long and connected at the ends to various objects such as water pipes. A counterpoise is available for erection when required. The counterpoise is parasitically tuned against ground as in Fig. 12 (b). The power input to the class C final of the transmitter is 50 watts and allowing for 70% efficiency, is approximately 35 watts input to the antenna.

The values of resistance in each case were initially determined by $W \div I^2$, as described in Part Two. Later, measurements of both resistance and reactance were made using a Wayne Kerr type B201 bridge. An attempt was also made to make measurements on a Q meter but it was found that there was too much interference from the antenna. In general, the R values were higher than those measured by the bridge, suggesting that the estimation of power input may have been too high.

The value of resistance was found to be difficult to measure in the case of the balanced horizontal. This was because the resistance is the minor component and is more difficult to measure, and also the bridge was not balanced to ground. The values shown here were measured on the bridge except the resistance of the doublet which was calculated from $W \div I^2$. If the bridge was correct, it would make the value of R about 10 ohms.

The following were the values determined for the purpose of calculation.

The antenna with feeders in parallel:
R = 23 ohms.

X = 135 ohms (850 pF.).

As above, but with a counterpoise:
R = 77 ohms.

X = 173.5 ohms (501 pF.).

Fed as a doublet:

R = 62 ohms.

X = 658 ohms (132 pF.).

Calculations for the

Vertical Antenna

Series-Parallel Conversion.—In earlier sections, series-parallel conversion was referred to. It is interesting to consider this conversion although details here are not given and only the first case is considered.

Series resistance = 23 ohms

Series reactance = 135 ohms.

These values would be represented by the equivalent series circuit of the load Fig. 3c.

By applying the standard formula (Ref. 5):

Parallel resistance = 814 ohms

Parallel reactance = 139 ohms.

These values would be represented by the equivalent parallel circuit Fig. 3c.

This means that if the antenna was tuned by a series reactance Fig. 11a, the load presented to the line would be 23 ohms. If a parallel tuned circuit was used, such as Fig. 11d or e, the resistance of the load in parallel with the coil would be 814 ohms. To match

a 50-ohm line, the turns tapping would be in the ratio $\sqrt{814 \div 50} = 4$ to 1.

Efficiency Case 1.—The antenna with feeders in parallel:

Electrical length of half top ($\lambda/4 = 1$) = 0.312.

Equivalent electrical length of top (Fig. 10) = 0.52.

Electrical length of vertical section = 0.222.

Form factor (from Fig. 7) = 0.91.

From equation (6):

$R_a = 98.75 (0.91 \times 0.222)^2$

= 4.03 ohms.

Electrical distance of feed point from the end of the antenna:

$0.52 + 0.22$

= 0.74.

The accuracy of the efficiency calculations and the application of the graphs depends largely on whether this point, 0.74, is correct. As pointed out earlier, it can be checked from the known reactance at the point being considered.

From Fig. 9 at 0.74, X = 250. This is not a good agreement but when calculated for a point where X = 135, R_a would be 4.2 ohms. Not a large difference in this case.

From equation (8):

Efficiency = $4.03 \div 23$

= 0.173 (17.5%)

Loss resistance = $23 - 4.03$

= 19 ohms.

Case 2.—In the case of the antenna with the counterpoise connected, R_a and X should still be the same but since the counterpoise is above the ground the length of the radiating section was 3 ft. shorter vertically.

Equation (6): $R_a = 3.28$ ohms.

Efficiency, equation (8) = 0.43 (43%).

If this result is correct it would suggest a 4 dB. improvement when using the counterpoise. From on-air checks, estimates of improvement vary from very little to 2 S points. Although these readings are not conclusive, the results indicate a worthwhile improvement.

The Effect of the Horizontal Section.

Many find it difficult to believe that the horizontal section of the antenna adds nothing to the radiation even when the top is larger than the vertical section. Some mistakenly refer to a "T" or an "inverted L" as a horizontal and think that the direction of the antenna will affect the radiation pattern. Although the top of the antenna produces no useful radiation it does greatly increase the efficiency. The loss resistance for the original "T" antenna was calculated to be 19 ohms. If the top was removed the loss resistance would be at least as high.

Radiation resistance with the top = 4.03 ohms.

Radiation resistance without the top:

F for a 0.222 vertical (Fig. 7)

= 0.505

From equation (6):

$R_a = 98.75 (0.222 \times 0.505)^2$

= 1.24 ohms.

Efficiency = $1.24 \div (1.24 + 19)$

= 0.061.

Compare this with the "T" antenna with an efficiency of 0.208, the improvement with the top section added would be 3.3 times (i.e. 3.3 times the radiated power).

Calculations for the

Horizontal Antenna

The length of one leg of the top

= 42 ft.

Electrical length of top ($\lambda/4 = 1$)

= 0.312

Form factor (Fig. 7) = 0.51

From equation (11):

$R_a = 197.5 (0.312 \times 0.51)^2$

= 5.0 ohms

Electrical length of feeder = 0.222

Electrical distance from end of antenna to tuner = $0.222 + 0.312$

= 0.534.

Refer to the graph of Fig. 14, the radiation resistance calculated above can also be obtained from the dotted curve (point 1). The resistance at the end of the line can be found by continuing along the graph to electrical distance 0.534. The resistance at this point would be 1.9 ohms—point 2 on Fig. 14. From measurement, the resistance was actually 6.2 ohms. If we take 6.2 ohms at point 0.534 (point 3), this corresponds to a resistance at the centre of 16 ohms (point 4) and an a.w.r. of 180. If the ground were perfectly conducting the resistance should be (from Fig. 15):

$5.0 \times 0.093 = 0.465$.

To sum up the following emerges:

Radiation resistance above perfect ground = 0.465 ohm.

Radiation resistance in space = 5.0 ohms.

Actual resistance = 16 ohms.

The actual effect of a poorly conducting ground is impossible to determine. Is it possible to apply the same method for determining efficiency as for a vertical antenna? That is: efficiency = theoretical radiation resistance + actual resistance.

In the case being considered,

Efficiency = $0.465 \div 16$

= 0.029 (2.9%).

As with the vertical antenna a check was made to see if the measuring point was as calculated. To check this, the reactance can be obtained from Fig. 9 at point 0.534 as 530 ohms, which compares with 658 ohms (measured) which corresponds with 0.47 from the end. This represents an error which, if correct, would make little difference to the feed point resistance calculations. It probably indicates that the antenna proper had a characteristic impedance greater than 600 ohms.

Comparing the efficiency of the horizontal with that of the vertical, the result is:

$0.029 \div 0.175$

= 0.165.

Some results obtained from reports when comparing the horizontal with the vertical for transmitting were as follows:

(Continued on Page 15)

OBITUARY

AIR COMMODORE ALFRED GEORGE FITZHEE, C.B.E., VK3VX

It is with the very deepest regret that the Federal Council and Executive records the passing away suddenly of Air Commodore Alfred George Fitzhee, C.B.E., VK3VX, on Friday, 2nd July.

After his retirement a few years ago from the active list of the R.A.A.F., he decided to take Amateur Radio and was helped by his great friend, Dr Alton Butement, VK3AD, towards obtaining the licence. George started on the air regularly since then, with fresh fields on 2 metres to explore on his return from Japan a few months ago.



George came on to Federal Executive early in 1967, firstly on Intruder Watch activities and later with the I.T.U. portfolio. An early article on this subject by him appeared in "A.R." of July 1967. Since that date he had been keen and active in Federal affairs and it is a tribute to his great personality that all the members of Federal Executive attended the funeral and wreaths were sent from afar.

Born in Victoria, George was 62 years of age, having devoted his life to the R.A.A.F. which he joined on passing out from Duntroon. From the beginning of the war he was concerned with radar and was the prime mover in setting this up in Australia and in Darwin and the North in particular during hostilities. After the war years had passed into memory he became Superintendent of the Woomea rocket range and held this post for several years. It was under him that so many social and general activities blossomed in that place. He himself even took to painting with water colours a la Churchill.

A grand personality. He will be sadly missed by all who knew him.

CHARLES FRYAR, VK2NF

It is with deep regret we report the passing on of this true Amateur on Friday, 2nd July, 1971. He was an excellent operator on both phone and c.w. At one time he won the W. T. Crawford Trophy as a Morse operator.

He was well known and respected on and off the air. He was well known on 2 metres and it was a joy and enlightenment to QSO him on this band.

He was one of the greatest givers of all times, both with his knowledge and bils and pleasure, and was very interested in QSO operations as some of his friends can tell.

Charlie was a licensed Amateur since 1930 and was very active until a couple of years ago when he became too ill to use his gear. He was the instigator of the Gladwinville and District Radio Club, started in 1937.

INTRUDERS

No complaints - no interference so they stay put!

ANTENNA FOR 160 METRES

(Continued from Page 14)

Distance 30 miles (no surface wave path): horizontal 2 S points better than vertical.

Distance 100 to 150 miles: on some occasions equal, better or worse.

Distance 500 miles: horizontal between 1 and 3 S points down on vertical.

It would appear that the distance where signals were equal from the two antennas is between 100 and 150 miles. From Fig. 16 the distance should be between 200 and 230 miles. This may indicate that the horizontal was even less efficient than calculated! The actual results were rather variable, suggesting considerable differences in conditions, but the final results would appear to confirm the calculations so far.

Fantasy

The rather rash assumption that efficiency for a low short horizontal can be worked out by such a simplified formula would appear to work out in this case. The assumption can be broken down into further assumptions.

Loss resistance in a lossless wire above a lossy ground equals radiation resistance above a perfectly conducting ground plus induced loss resistance above a lossy ground.

In most cases of a short low antenna above a lossy ground where the wire is also lossy, the induced loss will be the greater. A further rash assumption is made. It is likely that the resistance of a lossless antenna above a very lossy ground will be somewhere about its free space resistance, leading to the further rash breakdowns. Efficiency of a lossless antenna above a lossy ground = resistance above a lossless ground + radiation resistance in free space. Therefore actual efficiency of a horizontal antenna = radiation resistance above a lossless ground ÷ (radiation resistance in free space + wire loss resistance).

Note.—It is not intended that the above should be applied to a high, resonant antenna.

From the latter rash formula it is apparent that the efficiency cannot be greater than the ratio given in the former formula.

The above rash conclusions are offered as a guide to anyone who wishes to test them in practice. If anyone can provide a complete practical analysis of the above they are welcome to try, but who but a Radio Amateur would try to use a short low antenna above a lossy ground.

Conclusions from Results

1. The efficiency of a vertical antenna is fairly easy to determine.

2. It is suggested that the efficiency of a horizontal antenna can be determined in a similar manner.

3. The results have been cross checked with results in practice and would appear to be correct.

4. The comparison between the efficiency of the horizontal and the vertical is useful in determining the area in which the horizontal would have advantage over the vertical.

5. In short range work, outside the surface wave area, it is greatly advantageous to have a choice of a vertical, or a horizontal antenna. The doublet centre fed with open wire feed line provides the best answer since it can be used in either configuration.

REFERENCE

3. Radiotron Designers' Handbook Conversion from series to parallel impedance, p. 137

ANTARCTICA RESEARCH

Further to the paragraph in July "A.R." page 32, the tentative programme for the proposed Symposium includes (a) a review of communications requirements and statement of main practical difficulties affecting fixed and mobile (including position determination by radio) services within Antarctica and externally thereto and therefrom; (b) operational technical problems (co-ordination, maintenance, antennas, noise, snow static); (c) review of advantages and disadvantages of various transmission media (all frequencies and scatter) and use of satellites; (d) scientific results and developments likely to improve Antarctica communications and consideration of papers thereon (predictions, scatter, propagation, antennas in snow, poor earth, unmanned stations, modulation and data systems, etc.), and ending with policy and cost discussions and recommendations.

INDONESIA LICENSING

Notes from VK2AOK received from YB6BY

The Central A.R. organization is:-
Organisasi Radio Amatir Republik Indonesia (O.R.A.R.I.)
Jl. Lembang 45,
P.O. Box 2781, Djakarta,
Republic of Indonesia.

YB0—The capital Djakarta.
YB1—W. part of Java Is., Box 988, Bandung.
YB2—C. part Java Is., C/o YB5AG, Semarang.
YB3—E. part Java Is., C/o YB3BT, Surabaya.
YB4—S. part Sumatra Is., C/o YB4GA, Palembang.
YB5—W. part Sumatra Is., C/o YB5AI, Padang.
YB6—S. part Sumatra Is., C/o YB6JA, Medan.
YB7—Borneo Is. (Indonesian part)
YB8—Moluccas Celebes, etc.)
YB9—Bali to West Irian.
* Addressed as available

LICENSED AMATEURS IN VK

MARCH 1971

| | Full | Lim. | Total |
|------|------|------|------------------|
| VK50 | 11 | | |
| VK31 | 56 | 20 | 113 |
| VK32 | 1603 | 671 | 1874 |
| VK33 | 1319 | 632 | 1971 |
| VK4 | 830 | 187 | 717 |
| VK5 | 818 | 234 | 732 |
| VK6 | 361 | 137 | 498 |
| VK7 | 580 | 86 | 666 |
| VK8 | 25 | 14 | 40 |
| VK9 | 91 | 10 | 101 |
| | 4502 | 1811 | 6313 Grand Total |

W.I.A. BROADCASTS

7145 KHz

VK2WI, Sundays, 1100 hrs EAST
VK3WI, Sundays, 1030 hrs EAST
VK4WI, Sundays, 0900 hrs EAST
VK5WI, Sundays, 0900 hrs EAST
VK6WI, Sundays, 0930 hrs WEST
VK7WI, Sundays, 1000 hrs EAST



AUSTRALIAN FLYING CORPS No. 1 SQUADRON IN EGYPT 1917

In foreground, with cane, is Major Richard Williams, who will be giving the opening address for the R.D. Contest as Air Marshal Sir Richard Williams, K.B.E., C.B., D.S.O., R.A.A.F. (ret'd)
(Photograph by courtesy of R.A.A.F.)



3 SQUADRON AMATEURS AT RICHMOND, N.S.W., 15th July, 1940

Back (left to right) John Parr, VK3OM, Ned White, VK2HA, Ron Horne, VK4RR; J. Perce, VK2PE
Centre Frank Carey, VK2AM; Bill Smith, VK2BS, George Fenton, VK2GV, Snow Campbell, VK3MR,
George Cull, VK2AJB/VK2NO (Silent Key), Jim Edwards, VK2AKE
Front: Ken Williams, VK2XD; Arthur Wignell, VK2ALK (Silent Key); Rex Corthorn, VK2VG, now
VK3VG; Vic Jarvis, VK2VJ (Silent Key), Ern Calt, VK2FU, Daddy Gibson, VK2GH; and
Geoff Thornton, VK2UP
Not in photograph Ted Aked, VK2AEU; Tim Teehan (2L) (Silent Key)

LOW DRIFT CRYSTALS

★

**1.6 Mc. to 10 Mc.,
0.005% Tolerance, \$5**

★

**10 Mc. to 18 Mc.,
0.005% Tolerance, \$6**

★

Regrinds \$3

THESE PRICES ARE SUBJECT
TO SALES TAX

**SPECIAL CRYSTALS:
PRICES
ON APPLICATION**

MAXWELL HOWDEN

15 CLAREMONT CRES.,
CANTERBURY,
VIC., 3126

Phone 83-5090

LOG BOOK

AVAILABLE IN TWO TYPES—
VERTICAL OR HORIZONTAL

**Larger, spiral-bound pages
with more writing space.**

Price 75c each

plus 25 Cents Post and Wrapping
Obtainable from your Divisional Secretary,
or W.I.A., P.O. Box 36 East Melbourne
Vic., 3002

MARCH 1971

VK5ZFY - F. Richelieu, 12/12 Howard St., Underdale, 5032
VK3ZLJH - H. I. Day, 7 Piccadilly Circuit, Colonel Hill Gardens, 3041
VK6BX-B. A. Cook, 28 Pier St., East Fremantle, 6158
VK6JX - J. G. H. Hann, 46 Cape St., Osborne Park, 6017
VK6MJJ - J. K. Millband, 11 Salisbury St., Cottesloe, 6011
VK6ZBB - W. E. Olson, Lot 8, Morrison Rd., Upper Swan, 6055
VK7GW - G. W. Wood, 8 Norwood Ave., Leaton, 7250
VK7ZGT - G. L. Thomson, 131 Westbury Rd., Leaton, 7250

CANCELLATIONS

VK2BSP—S. N. Graves. Now VK1SR.
VK2AFD—A. O'Donnell. Now VK4QC.
VK2AUO—W. G. Hayner. Now VK2WZ.
VK2AUF—F. Flanagan. Now VK3CR.
VK1A10—W. Yates. Now VK3CS.
VK1A1Y—B. Dorris. Now VK3ZU.
VK2A10—R. Hooper. Now VK3LH.
VK3BFB—Geelong Amateur Radio Translator
Group. Now VK3GLR/2.
VK1Z30—E. Ewens. Not renewed.
VK4EP—P. Ellis (Rev Bro.) Transferred to Vic.
VK4GZ—E. M. Waddle. Deceased.
VK4GZ—W. R. Laughlin. Deceased.
VK4PM—J. G. Porter. Not renewed.
VK4XL—D. D. Kinnisley. Not renewed.
VK4ZLL—L. Labrugue. Transferred to N.S.W.
VK4ZTC—J. Crane. Transferred to Vic.
VK5AN—J. W. Emmel. Not renewed.
VK5AZ—R. S. Smith. Not renewed.
VK5DZ—M. J. Groth. Transferred to N.Z.
VK5JY—J. N. Cumbe. Not renewed.
VK5KZ—C. Simms. Not renewed.
VK5ZWR—W. R. Chapman. Transferred to
N.S.W.
VK6PR—P. Smith. Transferred Interstate.
VK6IW—A. F. Wreford. Not renewed.
VK6JT—A. C. Gray. Not renewed.
VK6YL—A. Clowes (Mrs.). Not renewed.
VK6ZL—J. J. Haines. Not renewed.
VK7JF—J. E. Forster. Now VK3CDX.
VK7ZFM—F. Richman. Now VK5ZFV.
VK7ZL—J. E. Forster. Not renewed.
VK7ZGW—G. A. W. Wood. Now VK7GW.
VK7ZNR—A. N. Richardson. Transferred to Vic.
VK7ZNR—J. E. Forster. Transferred to N.S.W.
VK8DS—D. C. Skeen. Not renewed.

APRIL 1971

VK3ZYL—R. A. Pinner, 13 Sheeles St., Dandenong, 3175.
VK4XN—H. M. Rone, 66 Ronemont Ave., Mosman Park, Surfers Paradise, 4217.
VK4UM—K. S. Morton, 17 Crown St., Tooowoomba, 4356.
VK4XG—G. S. Smith, 181 Stanhill Dr., Cheverton Island, Surfers Paradise 4217.
VK4ZHT—V. Husia, 3 Elmfield St., Upper Mt. Stuart, 4600.
VK4ZHN—N. H. Eberhardt, 75 Figtree Pocket Rd., Chappel Hill, 4069.
VK4ZNM—N. Boland, 44 Birch St., Cairns, 4870.
VK5DA—D. G. Ashin, 65 Wehl St., North Mt. Gambier, 5285.
VK5PJ—J. R. Smith, Youth Radio Club, P.O. Box 19, Port Augusta, 5700.
VK5PV—V. J. Roon, Flat 218, Keckwick 2-B, Wirrawarra, Keonemia, 5720.
VK5QA—F. T. Wilson, 3/23 Airport Rd., Brooklin, Port, 5332.
VK5UH—U. L. F. L. Flat 257, Block 2-B, Carinya St., Woomeera, 5720.
VK5UG—D. E. Wikstrom, Weapons Research Establishment, Moss Club, Woomeera, 5720.
VK5UH—F. V. Hughes, 58 Preston St., Como, 5800.
VK6HV—H. K. F. Van, 86 York St., Tuart Hill, 6066.
VK6II—J. M. DX Club of W.A., C/o News Sec., 12 Munyard Way, Morley, 6062.
VK6JZ—J. Garratt, C/o. 97 Hennessy Ave., Perth, 6005.
VK6OD—D. E. Pfiringer, 23 Kennedy St., Exmouth, 6707.
VK6OZ—O. R. Stanton, Lot 2, Ivanhoe St., Morley, 6062.
VK6PS—Perth Modern Senior School Radio Club, Roberts Rd., Subiaco, 6005.
VK6SU—L. A. Clait, 10000th Ave., Newacom Stn., Exmouth; Postal P.O. Box 20, Exmouth, 6707.
VK6WQ—W. J. Macross, 33 Caladenia Way, Keonemia, 5055.
VK6ZBT—C. J. Duddington, Station: White Rd., Narrogin, Postal P.O. Box 181, Narrogin 5213.
VK6ZF—R. J. Wynn, 85 Clayton St., East Fremantle, 6157.
VK7ON—O. R. Smith, 332 West Tamar Rd., Riversdale, 7252.
VK8GY—T. G. L. Tullett, 1/8 Hong St., Alice Springs, 5171.
VK8SS—S. A. Stephens, 55 Carruthers Cres., Alice Springs, 5150.
VK9AZ—Z. J. Smith, Telegraphs Training College, Roper Creek, Roper Creek, 5150.
VK9JM—M. R. Meehan, Montport Mission, Klung, W.P. T.F.N.G.

CANCELLATIO

VK2OZ - A Vanston New VK6OZ.
VK2RZ R. W. M. Custer Deceased
VK2AS - R. W. Bradbury Transferred to
Vic
VK2BQ - A Greenberg New VK3HYK
VK2BQ - A Greenberg New VK3BEO
VK2ZNP - W. T. Rine New VK3BTR
VK3CN - C. Wallers Not renewed
VK3CW - L. W. Not renewed
VK3FAE - F. H. Fuxander Transferred to NZ
VK3JAW - E. A. Williams Not renewed
VK3JBE - E. Williams Not renewed
VK3MCR - H. G. Austin Not renewed
VK3RCH - J. E. Bevers Mrs. J. New VK3JB
VK3RCH - J. E. Bevers Not renewed
VK3ZVT - D. S. Thomas Transferred to A.C.T.
VK4 - L. Moody Not renewed
VK4FW - L. R. Wofford Deceased
VK4BQ - C. P. O'Brien Not renewed
VK4BR - R. H. Morrison New VK4UM
VK4ZD - W. D. Not renewed
VK5GT - P. Gardner Not renewed
VK5GT - P. Gardner Transferred to A.C.T.
VK5QE - R. G. Gu... Not renewed
VK5ZER - D. G. Aslin New VK5DA
VK5ZL - R. D. Cline Not renewed
VK6TG - E. C. Gable Not renewed
VK6ZG - R. H. Modern Senior High School
VK7HO - H. E. Rogers Not renewed.
VK8GZY - G. L. Tillett New VK8GY
VK8GZY - A. R. Stephens New VK8SS
VK9QA - N. A. Miller Returned to main unit

R.D. CONTEST

14th and 15th AUGUST, 1971

ALL SET TO GO

Opening address by Air Marshal Sir Richard Williams, KBE, CB, DSO, RAAF (Retd)

A BRIEF SPECIFICATION . . .

INOUE SOLID-STATE 2 METRE F.M. TRANSCEIVER

MODEL IC-20 \$295 inc. S.T. + Two Channels

TRANSMITTER: Frequency coverage: 144 to 148 MHz. 12 Channels. Deviation: ± 15 KHz. Power: 20 watts D.C. Input. Microphone: Dynamic. Antenna switching—no relays—all solid state.

RECEIVER: Sensitivity, 0.35 μ V. for 20 dB. quieting. 1st i.f., 10.7 MHz. (two ceramic filters); 2nd i.f., 455 KHz. (one ceramic filter). Xtal oscillators, both rx and tx individual trimmer

Dimensions: Height 2 $\frac{3}{4}$ ", width 6 $\frac{1}{4}$ ", depth 7 $\frac{1}{4}$ "; weight 4 $\frac{3}{4}$ lbs.

Operation: 12V. D.C. A.C. Power Pack with Disc. Meter optional extra.

WRITE! for copy of "QST" review, Jan. 1971. CALL! for inspection.

See and hear at:—

INDUSTRIAL & MEDICAL ELECTRONIC CO.

6th Floor, 288 LIT. COLLINS ST., MELBOURNE, VIC. Phone 63-9258, A.H. 848-3018

COMING! 430 MHz. SOLID STATE TRANSCEIVER, C.W. KEYERS, MONITORS, MIC. COMPRESSORS, MOBILE ANTENNAS.

REMEMBER! INOUE for the finest Amateur and Commercial V.h.f.-U.h.f. Communications Equipment.

WAYNE COMMUNICATION ELECTRONICS

Catering specially for the Amateur with Components, Receivers, Transmitters, Test Equipment. Everything from Resistors to 100 MHz. Frequency Counters

ALL AT UNBEATABLE PRICES

- **COLLINS ART13 AUTO-TUNE TRANSMITTER.** 2-18.1 MHz AM or CW. 813 PA, 2 x 811 Modulators. Complete with all tubes. In good condition. \$30 each. Freight forward.
- **COMPUTER BOARDS.** Removed from functional equipment. Contain 4 VHF transistors, 12 high speed switching diodes, 2% metal oxide resistors. \$1.50 each.
- **CERAMIC 1625 SOCKETS.** Suit also 3AP1 CRO tube. 15c each.
- **POWER SUPPLIES.** 230v. 50 Hz. input, 300v. 100 mA. DC output. Manufactured by A & R. Brand new. \$10 each.
- **WIRE WOUND RESISTORS.** Range: 1.8 to 620 ohms. 6 watt. New. 5c each.
- **SPECIAL! TRANSFORMERS:** Primary 230v. 50 Hz., Secondary 27v. 3 amp. This month only. \$3.00 each.

All items plus pack and post.

Come and inspect the full range of equipment and components at

WAYNE COMMUNICATION ELECTRONICS

757 GLENFERRIE ROAD, HAWTHORN, VIC., 3122

Phone 81-2818

Overseas Magazine Review

This is different but it uses material supplied by VK3ASC and VK7RC. Any comments? See end for key.

ANTENNAE: Simple vertical arrays (4); plain facts for tyro and beginner (also feeders and trans-matchers) (6); wet string fiasco (7); 160 mhz centre-tapped whip (17); compact verticals (18); portable (4); Kitz helical beam (11); G4ZU single boom (10); 2 mhz parallel fed vertical collinear (9); microwave paraboloids (2).

MASTS: A-frame (4); 10 extra feet on the tower (12).

ROTATORS: Simple (perhaps too simple) (1); delayed action braking (8).

CHANGE-OVER APPL. Sol. state switch (8).

TRANSMITTERS: Beginners' 1-valve high power (7) translator 12w, for 10 mhz (12); solid state 10 mhz d.s.b. (12); power level comparisons (15); p.c.b. ATK-2 modulator (18); lazy man's v.f.o. for 2 mhz (11); stability without xkls with solid state modulator (12); "rubber" state (18); digital proportional radio control (10); advanced pre-amp compressor clip-

per (12); power FETs (15); tripler 70 cm. (17); tripler to 23 cm. (18); 160 mhz s.s.b. transmitter from 40 mhz (18).

RECEIVERS: Latest techniques in new design "plagiatorise and hybridise" (2 to 5); direct conversion heterodyne (8); freq. counter (6); xtal calibrator (12); Drake 23 mod. for 160 mhz (17); R155 modernising (18); ARSS S meter (3, 5); SE303 review (10); r.f.l.v. converter (6); re-winding old rx (11); xtal WWV for Swan Cygnit (9); FET for a.m. b.c. rx (6); noise blankers (8, 12); solid state preselector (12); PEP dual gate pre-amp. for 2 mhz (18).

TRANSISTORS: One-tube cheap 2 mhz (12); ZLEDBB triblers (8); 2 mhz fm (12); SIC for s.s.b. and a.m. (5); HW100 mods. (11); H23 handi-talkie mods. (12); FT200 review (11); Drake TTS break-in c.w. mod. (13).

AMPLIFIERS: Switching remote linear (13); low power design concepts (13); high power for 80-160 mhz (15); higher power tripler for 70 cm. (2); 500w 2 mhz pentode linear (9); grounded grid pair 813s (3); using SL60/12 r.f. (1); ensuring transistor stability (1).

REPEATERS: (12 to 15).

KEYERS: IC (8, 17); touch-coder one-letter memory (8).

POWER SUPPLIES: Auto current overload protection (8); solid state protective devices (10); SCR regulated (19); dual input design (8).

TEST EQUIP. All mark tester (12); simple r.f. wattmeter (7); simple freq. std. (4); noise generator (12); fm low cost vxo signal source (12); meter evaluator (12); simple a.w.r. device (18); r.f. magnetometer and f.a. meter (10, 11).

F.W.M.: Newcomer tips (10); advantages (12); U.S.A. side (12); transmitter directory (18); simple circuit (18); simple varactor modulator (12); s.b. 455 KHz discriminator (1).

MOBILE: Camper installation (10).

INTERFERENCE: Recognising f.m. intruder signals (6, 17, 18).

T.V. Slow scan techniques (11).

PROPAGATION: Tropospheric 2 mhz study (18).

SATELLITES: Reception (2, 18, 17).

MICROWAVES: (1 to 8, 12, 18).

COMPONENTS: Variable capacitor do's and don'ts (2); compact band-pass filter for 2 mhz (5); low pass filter for F.D. (8); tuning diodes (8); v.f.t./u.b.f. practical coil winding data (13); ferrite inductors (18); DIY "computer" (18); f.m. net alert bell (11).













OTHER: Rhnd operators' aid (11); graphs of power, volta, impedance (15); FET symbols (19); cheap 24-hr. digital clock (8); dry cells re-charger (looks interesting) (8).

KEY (all are 1971)

"Radio Communications". Feb. (1), Mar. (2), Apr. (3), May (4), June (5).
"QST". May (6).
"Break-In". Apr. (7), May (11).
"CQ". Mar. (8), Apr. (10), May (11).
"3". Apr. (12), May (13).
"Ham Radio". Mar. (14), Apr. (15).
"Short Wave Mag.". Feb. (18), Mar. (17), Apr. (18).
"Aust. E.E.B.". Mar.-Apr. (19).

PREDICTION CHARTS FOR AUGUST 1971

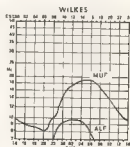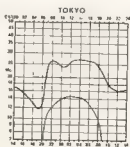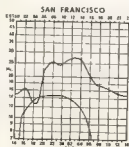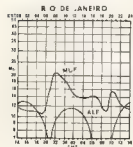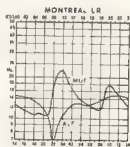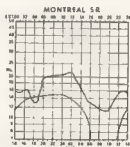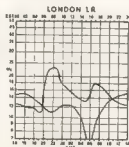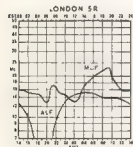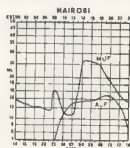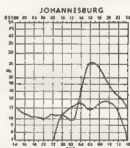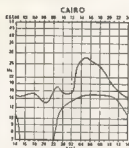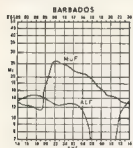(Prediction Charts by courtesy of Ionospheric Prediction Service)



OBSERVATION POST

By H. F. Everett

We seem to have very little exchange of news about visiting Amateurs to our shores. Is this symptomatic of something? Extremely knowledgeable and interesting recent visitors who come to mind are WA6PSC (VR5DK, ZL1ATC, 3BDEK), ZL2AMJ, VP9DC, G3UJB, G2FUX, C8RDR, SM5DEQ, VU2JD, VU2OV and K2IXP.

Perhaps, of greater interest to the reader than those who have been here are those who will be visiting Australia. There is, then, a fair chance that we can welcome our visitors with a measure of hospitality, twist their arms to give a group talk perhaps and generally to exchange a yarn or two. Is there a feeling that news of visits must be jealously guarded?—"He is my friend, I will not share his company with any Tom, Dick or Harry"; "I alone will take pleasure in sharing his pleasures of new scenes and fresh faces". Or is it perhaps apathy? "I have my own group of friends, to heck with strangers." "Too busy." Sky? Afraid of him patting your pocket-book perhaps?

Most of us were brought up in the true Amateur spirit. Is there any real difference between talking to "Bob" over the air and an "eye ball" when he is a visitor? If you visit Timbucto or Athens, would you like to meet the local Amateurs in a friendly way?

Would we, therefore, like to have news of visitors who plan to be with us for a brief moment in time? As a starter, a panel is appended. Why not write in when you know about visitors shortly to arrive. Many of us can then join in with a welcome of some kind—be it ever so humble.

Although the Amateurs' interests seem limitless, many of the DX fraternity speak in glowing terms of our wonderful country. No better tourist ambassadors could be found anywhere. In this way they take pleasure in persuading overseas Amateurs to visit Australia or even local Amateurs to visit places they would otherwise bypass. Very excellent contacts are made, good friends are acquired and the talk even encompasses such things as the unique quality of the red and black soils of the Downs.

Some people have asked if we can and should do more. For example, sending to ships and radio officers aboard ship a printed note of how to contact a local Amateur or local groups for the benefit of the travelling Amateur. Most of these would welcome a few hours ashore next to a rig in congenial company or even some advice on what sight-seeing should be done. Most of them would jump at the idea of a contact "back home". Is there a need for a visitors' column? Write to the Editor and we shall soon see.

VISITING AUSTRALIA

9J2HE—During September

M.V. "Canberra"
Perth, eastwards

GOLDEN JUBILEE

**Congratulations! and Many More
Happy Days to VK4DO for 50 Years
in Amateur Radio**



Hal Hobler, North Rockhampton, built his first crystal set in 1921 and has progressed from a 1923 10-watt 240 metre R/T rig made out of completely home-made components (except the valves) using a coupled Hartley oscillator and loop (absorption) modulation right through to the present day s.s.b. gear with home-brew power supplies.

The receivers included a "lo-iso" 2-valve model with a quarter inch plate glass panel, the holes of which had to be drilled with rat-tail files.

Antennae in use are a 2 el. quad for 14 MHz., a dipole for 7 MHz. and a 3 el. yagi on 53 MHz. which, with a converted ex taxiphone, is used for JA contacts when openings occur.

Hal considers the W.A.Z. certificate the highest award in Amateur Radio —he has three: c.w., a.m. and s.s.b.

In 1926 he made two-way contacts with the U.S.A. using 140v. on a 201A rx tube and was heard in ZL on phone. W.A.C. in 1936 was made in 50 minutes with 48 watts and on phone in 1948 in 28 minutes.

The holder of numerous Awards—going back to 1924—Hal is active in the R.D. and VK-ZL contests. His most difficult things to do in Amateur Radio? To copy a 500-word c.w. Trans-Pacific Test message in 1926 and to get QSL cards from Zone 23 before the JTs went there.

★

FEDERAL CONTEST COMMITTEE

For the past six years the Federal Contest Committee has been located in Perth, Western Australia under the leadership of the Federal Contest Manager, Neil Penfold, VK2ZJ. Neil and his group have done an excellent job as members will know, but the time has come for a change.

At the last Federal Convention the Queensland Division volunteered to take over the administration of our Contests and the VK4 Federal Councillor has now advised that his Division has appointed Peter Brown, VK4FJ, as the new Federal Contest Manager. Peter's address becomes:

FEDERAL CONTEST MANAGER.

G.P.O. BOX 638,
BRISBANE, QLD. 4001.

and logs for all local Contests will go to G.P.O. Box 638 for the next three years at least. However, VK5ZDK will, for the present, remain administrator for the VK-ZL Contest and consequently contestants should look carefully at the rules to determine the correct address for their Contest logs.

Hy-Q

CRYSTALS

FOR AMATEUR USE

A full range of high stability close tolerance crystals especially made for Amateur use is now available.

These crystals are made on the same equipment, with the same care, and subjected to the same exacting tests as those manufactured by us for Military and Industrial applications.

| | | |
|------------------------|--------------------------|--------|
| 100 KHz., 0.02% | Style QC13/X holder | \$9.00 |
| 300 to 500 KHz., 0.02% | Style QC6/C (D) holder | \$6.50 |
| 1000 KHz., 0.01% | Style QC8/A (D) holder | \$8.50 |
| 2 to 20 MHz., 0.005% | Style QC6/A (D) holder | \$4.70 |
| 20 to 60 MHz., 0.005% | Style QC5/A3 (D) holder | \$5.30 |
| 60 to 100 MHz., 0.005% | Style QC6/A5 (D) holder | \$5.95 |

Other frequencies and tolerances can be quoted for on request—send for technical brochure.

Postage/Packing:
Victoria 20c, other States 30c

The above prices are Nett Amateur to which should be added Sales Tax if applicable at the rate of 27½% for Receiver use, or 15% for Transmitter or Transceiver use.

Hy-Q

Electronics Pty. Ltd.

10-12 Rosella Street, Frankston, Vic., 3190

P.O. Box 256

Telephone 783-9611, Area Code 63.

Cables: Hyque Mcbourne Telex 31630

AGENTS

| | |
|---------|---|
| N.S.W.: | General Equipments Pty. Ltd., Artarmon. Phone 438-2705 |
| S.A.: | General Equipments Pty. Ltd., Norwood. Phone 63-4844 |
| W.A.: | Associated Electronic Services Pty. Ltd. Moorley Phone 79-3850 |
| N.T.: | Domestic Electronics Pty. Ltd., Darwin. Phone 6581. |

Correspondence

Any opinion expressed under this heading is the individual opinion of the writer and does not necessarily coincide with that of the Publishers.

NOVICE LICENCE

Editor "A.R." Dear Sir,
In the letter in July "A.R." from VK3RN, he makes a brief reference to frequency allocations proposed by the committee pressing for the introduction of Novice licensing. The reference is on page 127, para 3.
I would like to go much further than talking about 180 metres and amplify the remarks he makes on 180 metres to the other h.f. bands. To my mind, there has been complete "Novice" thinking by the committee, especially as they have been keen to use U.S. Amateur Radio as examples.
The recommendation of the allocation of the lower end of all h.f. bands is ludicrous, and surely is used to try and get the experienced DXers jammed into a small portion of the DX bands. If the committee say this is not so, let me make two points to show the impracticability of the proposal.
(a) On 3.5 MHz, for example, the Novice has 3500 to 3535 KHz, leaving the experienced DXer 3500-3505 only. If the regulations force the Novice that spectrum. The DXer will, of course, not be confined to that 5 KHz., and because he will have high class receiving equipment, unless very small, the noise will not cause him much trouble. On the opposite side, the Novice will probably have only a simple receiver, incapable of handling the amount of interference resulting from the DXer chasing his 5-band DXCC, or working his regular "skeds". The result he closes down.

(b) The present licensing procedure in the U.S. precludes thousands of Amateurs in the States from operating below 25 KHz. on any of the bands 1.5 to 20 MHz. Therefore Australian Amateurs, and of course, all other countries, will regularly be operating above the first 25 KHz. of any of the above bands and, accordingly, force the Novice, solely because of lack of experience and operating ability to close down. How much would he copy through a station operating at 25 w.p.m. or even higher.

In my discussion with Rex Black on Novice Licensing, at no time did he mention the frequency spectrum proposed for them, otherwise I would have pointed out the futility of proceeding with the idea that has emerged.
It amazes me to think that instead of encouragement to get on the bands, a proposal is made that will do nothing but discourage them to get on the h.f. bands, and as a result make for discontent.

— F. T. Hine, VK3QL

Editor "A.R." Dear Sir,
I have been following the discussions about Novice licences with interest and wish to place on record that I favour the introduction of this type of licence. Having read in another radio magazine about the general types of conditions which might be considered, I can easily see a Novice licence would use aid the

instruction which I provide to a local Y.R.C.S. Group.

First, I think that my holding a Novice licence as the Group Leader would add some prestige to my training efforts. Second, I can look forward to some of my class progressing to the Novice standard and joining with me in regular "skeds" and so gaining experience under my supervision before being left loose to contact other Novices and other Amateur operators. Third, I feel that lads who have had Novice training will turn out better than those who then start on their own. The A.O.C.P. under present licensing and examination conditions. Fourth, I can see the advantage of a Novice licence as a way for oddage people to enter the Amateur Radio hobby. Fifth, I think that the local adult radio club would benefit by increasing its membership if it contained a group of Novice operators as well as the present A.O.C.P. Limited (Z call), and S.W.I. members.

— Gordon Procter,
Y.R.C.S. Group Leader, Gosford.

Following is a précis of a letter from Mr. Karol Nod, ex OK5UH, of Sydney:

SPX BULLETINS

The SPX Bulletins are issued bi-weekly by the IUWDS World Warning Agency for Satellites at the World Data Centre A for Rockets and Satellites, Code 301, Goddard Space Flight Center, Greenbelt, Maryland, 20771, U.S.A., and are distributed regularly to the COSPAR National Spacewarn contacts for satellite information and to Satellite Warning Centres for their further distribution to interested institutions in their countries or regions.

Paragraphs A and B of these Bulletins are not being reproduced as they would duplicate the list given in Section 1 of the Survey of Satellites and Space Probes. Paragraph C hereunder contains information not previously published in the Bulletin. This information is being included regularly in each issue of the Bulletin.

"C"—SPACECRAFT PARTICULARLY SUITED FOR INTERNATIONAL PARTICIPATION (Category I)

1. Spacecraft with essentially continuous radio beacons on frequencies less than 100 MHz., or higher frequencies if especially suited for ionospheric or geostatic studies (* denotes new information).
Reference in COSPAR Info. Bulletins

| National Name | Frequency (MHz.) | |
|----------------------------------|--|-----------|
| 1968-032A Explorer 37 | Feb. 14, 1970: 30, 40, 41, 250 milliwatts; also 360 (100 milliwatts); also 163 and 234 | |
| 1968-110A ATS 3 | Oct. 11, 1970: 0000 UT at 148 825°W, 1.351°N, drifting 0.915°/day Inclination 2.846° | 37, p. 35 |
| 1967-111A ATS 3 | Oct. 11, 1970: 0000 UT at 63.544°W, 0.830°S, drifting 0.802°/day Inclination 1.117° | 44, p. 38 |
| 1968-002A Explorer 36 | 182, 234, 272 (300, 400 and 500 milliwatts) | 48, p. 41 |
| 1968-005B 1968-005A ESSA 2 | 136.77 at 380 milliwatts | 48, p. 43 |
| 1968-054A Aurora | 136.178 at 0.3 watt | 47, p. 33 |
| 1968-100B TTN 3 | 136.85 at 100 milliwatts | 48, p. 37 |
| 1968-110A OAO 2 | 136.441 at 160 milliwatts | 48, p. 38 |
| 1968-114A ESSA 3 | 136.778 at 380 milliwatts | 48, p. 39 |

2. Satellites which provide telemetered information on a continuing basis (* denotes new information).
Reference in COSPAR Info. Bulletins

| National Name | Freq. (MHz.) | Details |
|--------------------------|----------------------------------|---|
| 1968-016A ESSA 2 | 137.80 | Deactivated Oct. 10, 1970 |
| 1968-017A Explorer 37 | 136.321 137.560 (150 m.w.) | (x-rays) spin rate is 55-60 rev. min., aspect angle is controlled between plus or minus 10° |
| 1968-114A ESSA 3 | 137.630 | AFT-8-picture sequence starting at 54°N descending, providing coverage on entire sunlit portion of earth |
| 1969-037A Nimbus 3 | 136.95 | AFT has been programmed off due to spacecraft attitude problems |
| 1970-068A TXOS 1 | 136.77 137.2 | Tracking beacon (250 mW) AFT (5 watts) Up to an 11-picture sequence starting at 59°S ascending, providing coverage over the sunlit portion of the earth. An AFT station can receive up to four pictures in a single pass |

3. Optical objects used for geophysical studies. (Also suitable for air density studies). Additional research interest is indicated by † for gravitational field, and ‡ for rotational speed of atmosphere

| National Name | Priority | 191967-042A Ariel 2 | 191968-090A Cosmos 248 | 191968-108A Cosmos 316 | 191970-043B Cosmos 347 |
|----------------------------|----------|------------------------|---------------------------|---------------------------|---------------------------|
| 1968-046A NINN | 8 | 3 | 3 | 3 | 3 |
| 1968-001A NINN | 8 | 3 | 3 | 3 | 3 |
| 1968-032A Cosmos 44 | 8 | 3 | 3 | 3 | 3 |
| 191968-043A Explorer 36 | 8 | 3 | 3 | 3 | 3 |
| 1968-054A Explorer 36 | 8 | 3 | 3 | 3 | 3 |

4. Satellites useful for astronomical observation programmes with small cameras.

| National Name | Incl. (°) | Per. (h:m) | Ap. (cm.) | Magn | Remarks |
|------------------------|-----------|------------|-----------|--------|---------------------|
| 1968-046A NINN | 90 | 1070 | 1090 | Plus 4 | |
| 1968-001A NINN | 89 | 890 | 890 | Plus 5 | cylinder, 8 x 1.5 m |
| 1968-032A Cosmos 44 | 62 | 800 | 890 | Plus 4 | cylinder shape |
| 1968-070F Cosmos 5 | 56 | 1360 | 1510 | Plus 5 | rocket body |
| 1968-072F Cosmos 5 | 56 | 1390 | 1580 | Plus 5 | rocket body |
| 1968-054A PAGES 1 | 45 | 2840 | 5710 | Plus 2 | |

(With acknowledgment to COSPAR Bulletin, Dec. 1970)

W.I.A. VICTORIAN DIV.

V.H.F. RALLY

Sponsored by the VK3 V.H.F. Group

SUNDAY, 19th SEPT., 1971

GEMBROOK

In the beautiful Dandenong Ranges.
Location: Gembrook Sports Ground,
Cr. Orchard Rd. and Main Rd.
Programme: Events for the OMs.
XVLS & Harmonics. Lunch provided.

Cost. \$1.50 per Amateur/S.W.I.
Regist. on fees may be sent to and programmes obtained from
V.H.F. Group,
P.O. Box 36,
East Melbourne, Vic., 3002.



By H F EVERICK
C/o. P.O. Box 36, East Melbourne, Vic. 3002
(Times are in GMT.)

A plea for help. An answering call. But yours truly tackles this column this month without much aid from anyone at the time of going to press. Presumably everyone is DX'ing on the square-eyed monster!

During June there were enough DX-peditions to satisfy most of the avid DX hunters and July seems no exception either. VK3XP portable Willis Island by Larry Pace and his merry men set out in July "A.R. QSLs to K8RLV. Unfortunately sea conditions had deteriorated so much that the Melish Reef trip did not eventuate. Operations from Willis were on all bands and the operating was first class.

Darlene WA6FSC, etc., passed through Melbourne and Perth early in June on her way to Mauritius where she was active as 3B3DK for a short spell before embarking for Rodriguez Island where she activated 3B9DK from the last week in the month. Thousands developed with the 18 mx part of the rig and the signals on 30 mx suffered for a time until the antenna was hoisted higher. VK3XP is due to leave Rodriguez late in July to continue her safari to 524, 5X3 and the like. At the time of writing, a 224 call seems possible, but the 5X3 might be a little doubtful although, as the last few months licensing has been restored. QSLs to VK3AKV.

Mention of 5X3 reminds me that 5XANA is active from there. Uganda has become a rarity lately since the days of the VQ6s and even 524 (previously VQ6) and 5X3 (ex VQ6) are now almost as rare as the former French Colonies in Africa. From that area TQ7AA is heard sporadically on 80 very infrequent 912A, seldom any 812B and 5X4C, the occasional 805 but several CR6s, CR7s and ZEs.

Early in July the avid DXers had the pleasure of chasing Martin as 3C1ED on one island of Indonesia. Foo in the Gulf of Guinea. Other areas activated by him were to be Equatorial Guinea and the island of Annobon recently as 3C2ON.

Nearer home you will see elsewhere some notes on Indonesia. The addresses of some of the local representatives of O.R.A.R.I. are given as—

YB4G—R. Imam Purwito, DjI, Argopuro No. 4, Semarang.

YB4B—Mohammed Saleh, Gg. Sumatra No. 3-5, Palembang.

YB4J—R. Soegito, DjI, Ampers No. 2, Kumpus University, Sumut, Medan.

YCBT—Aryanto, DjI, Indragiri No. 62, Surabaya.

YD5A—Purneyn Ch, DjI, Pasar Raya No. 57, Padang.

Others shown on the lists were YB1s AG, AK, BH, YB4s AJ, AR, YB4D, YB4G, YB4C, YB4E, YB4H and YB4I. As for YB4F and CJ. The lists were sent on by VK2AOK, for which many thanks. It is noted that expatriate calls do not appear to have been listed. An examination of the current predictions shows that conditions on 10 mx will become extremely sporadic, 15 mx will probably be open most of the time during daylight hours. 20 mx should be open during the day, sometimes at night, and deep dips to fade-out around sunset and sunrise, 40 mx average during the day but opening by darkness—if you can find the holes between the intruders. 80 mx will be open during the day but only well to all VK and ZL areas and beyond by night, and finally 160 mx opening at night. Several VKs worked through to KL7CL on 160 mx c.w.

Ample DX is still available. On 80 we miss out on the DX which congregates around 3700 KHz. On 40 512XV and a G or two came through well. On 15, Ws and JAs are still plentiful, with 3B8CZ still consistent. On 20, there is ample DX for all and among the less frequent calls heard were JA3B1 EA8F7 (Box 66), Los Palmar, CN8CG KAREJ (list by 565A), PK3AC FORDS (JAs), and 512XV in is QSL JA1BA. K8BTD (Dept of Education, Pago Pago, Am. Samon, 68920), KXG9N, PYO DX-pedition to Trinidad is not yet heard. VP JA1, VP2V, ZD5F, ZL40I, JA on Campbell is, is QSL ZL40C, often on 80 mx, ZM7AT (QSL, K8RLV, YB4H, 3B1L, the Australian DX-pedition), is QSL WJN1J, SZAKI, 8F42Z, 9G1FF, 901BX, 9H5PSD Mary (QSL Box 795 Kuching, Sarawak), N1MIM (QSL K3FVQ, 8F4V, 9G1FF). QSL cards are now under circulation from the operation of VK0KB.

For FX hunters July should bring two new ones in KC2GMP, Great Mammoth Fair, Box 111, Freehold, NJ 07731, and KC0CK, Box 73, Shawnee Mission, Kansas 66201.

A letter received from Mac VK3NI on Norfolk Is., takes issue with June "A.R." being incorrect. He says there are three, not two, of the Amateur fraternity resident on the Island and it is a Radio Amateur's paradise, anyone using the bands when open can expect a pile up. The other two are of course VK3JZ and VK3RH. Incidentally, VK3JF worked from Norfolk Is. on 23rd May to 6th June and greatly enjoyed his visit. I gather he worked a.s.b. and c.w., obtaining W.A.C. on both and experiencing very courteous pile-ups on c.w. He also said that a VK3 reckoned VK3 Norfolk Is. was not DX! John used a 144VQ and reckons 4/5 weeks delay must be allowed for the issue of the licence.

For SWL's comes a note that the EDP system will introduce a change in the 5.w.i. number by the addition of a 9 between the State numeral and the existing three numeral personal number. Thus SWL-L7777 will become SWL-L9777. This assumes that the EDP system has been fed with the correct number. So there could be some changes in the numbers which, I am told, the EDP processing boys wish to avoid particularly where 5.w.i.s have had cards printed.

Are you anti-list, pro-list or don't care? It seems there are demonstrators against everything if the performance on the afternoon of 19th June is any criterion. This probably resulted in ZK1MA going QRT, much to the chagrin of an enormous pile-up of Ws awaiting their turn to be called in by 9R4P as MC. The demonstrator, a VK3, did not work ZK1MA then either. He was too busy calling the Ws head on. I gather a quick reference agreeing to let him in. Most DX chasers deplore any kind of financial list and any rare DX station working to such a list is soon to be in dire trouble. Most listeners who had heard the enormous pile up on ZK1MA's fixed frequency would not have failed to note the error of believing that was any financial listing—far from it. The old story of too many chasing too few.

If a rare DX spot is activated it would take it a year every minute of every day if 10 contacts per minute to work the other half million licensed Amateurs in the world. To work every licensed VK station it would take nearly three days without a break at the "insurance" rate of 100 QSOs per hour. Fortunately, not every Amateur is active, not everyone chases DX and not all are on the h.f. bands, but even so, the phenomenal pile-ups which occur for a rare one must be heard to be believed.

The good operator of the rare station works of his own frequency (much to the annoyance of the transceiver mob) and proceeds to peel off the layers with a professional touch. He wastes no time listening to stations busily calling out his own call sign. If you are in there he assumes you are after him. He likes the quick clear call, your own call sign, just once. This saves time and QRM. To be called in by him and then start telling him about your rig, name, antenna and general ragging aggravates all the other hopefuls in the queue.

Come along now. How about some news? What about the T 4-7 What has happened to our old faithfuls?



FEDERAL AWARDS

COOK BI-CENTENARY AWARD
The following additional stations have qualified for the Award:

| | | | |
|-----------|--------|-----------|-----------|
| Cert. No. | Call | Cert. No. | Call |
| 1256 | WHRJC | 1380 | WBDDI |
| 1257 | W82LGO | 1381 | W8XJL |
| 1288 | W5ZEEC | 1382 | PA3KGS/W2 |
| 1368 | AX8TE | 1383 | AX3YV |

V.M.F.U./U.h.I. Station

Cert. No. Call
28 AX42AM

N.W.V.F.C.C.

Cert. No. Call
30 VK4ZIM
194

W.I.A. SE MHL W.A.S. AWARD

New Member:
Cert. No. Call
95 VK9ZAW

BEAM IN or OUT..

For MORE DX

With a **Stolle**

Automatic Aerial Rotor

- Fingertip Control • Simple yet positive action gives "spot on" control of your antenna beam.

Full details on request (use coupon below).



EDDYSTONE EC 10 Mk II



NOTE THESE FEATURES

- "S" METER — carrier level meter.
- FINE TUNING Control.
- LOW-LEVEL output available for recording purposes.
- 550 kHz to 30 MHz in five ranges.

Send in coupon below for Technical Brochure.

ONLY AVAILABLE from

R.H. Cunningham
LTD.

VIC: 608 Collins St., Melbourne 3000.
61 2464

NSW: 64 Alfred St., Milsons Point 2061.
929-8066

WA: 34 Wolya Way Balga, Perth 6061.
49-4919

QLD: L. E. BOUGHEN & Co, 30 Grimes St., Auchanflower 4066, 70-8057.

| | |
|-----------------------|----------|
| STOLLE ROTATOR | A.R.8/71 |
| EDDYSTONE EC 10 Mk II | |
| Name | |
| Address | |

Sub-Editor: ERIC JAMIESON, VK3P
Farrington, South Australia, 5233.
Closing date for copy 30th of month.
All Times in E.S.T.

AMATEUR BAND BEACONS

VK0 53.54 VK0RZ Antarctica.
VK3 144.740 VK0VE Vermont.
VK4 144.380 VK0VAF 107m. W. of Brisbane.
VK5 144.500 VK0VAF 107m. W. of Brisbane.
VK6 39.05 VK0VAF Tuari Hill.
VK7 144.500 VK0VAF Tuari Hill.
VK8 144.500 VK0VAF Tuari Hill.
VK9 144.500 VK0VAF Tuari Hill.
VK99 144.500 VK0VAF Tuari Hill.
VK00 144.500 VK0VAF Tuari Hill.

No notified changes to beacon list this month although it would appear from a report in the Geelong Amateur Radio Association Club Newsletter that Phil VK0KX (ex VK3FF) is running a beacon on a 24-hour basis. Phil VK0KX, with the keyed W, call sign of VK0KX, Phil listens daily on 8-hours between 1900 and 2000 hours.

These notes are being prepared whilst on holiday in Alice Springs in VK8. They may therefore of necessity be incomplete and any correspondence arriving at the end of the month and the beginning of the next will find the weather is great, warm sunny days and cool nights. So far have not tracked down any h.f. info. but may be able to do so before I leave. At the last minute I decided against taking v.h.f. equipment with me owing to the weight and the gear required. When one considers the equipment needed would include complete 6 and 2 metre tx's and associated power supplies, converters, etc. and at least two yagi antennas of reasonable size, most, and these to be transported over 800 miles of generally rough unsealed roads, it is not surprising that the chances of any contacts whatever are as remote as either land mail or telegrams. This is a pity for operation. Therefore I have contented myself with bringing a small compact 40 mW rig lent me by VK45Q and which has provided some d.a.b. contacts over distances of 1,000 miles from about 10 watts.

METEOR SCATTER

Rod VK2EJQJ sent a further brief note to advise having successfully worked VK4RO on 2.8 m.b. by 3.4 m. on 28 Sept. This came from Rod's reward for diligently sticking to a skeed with David VK8AU in Tennant Creek which did not bear fruit. While on the subject of M/S, in a very round-about way from Rob VK3AOT comes news that Wally VK2ZW has added another State to his list of M/S by working George VK3ASV during June, Congra. Wally, but what about some notes of your general activity in this direction please.

From the pen of Bob VK3OT, my most esteemed friend from VK3, comes advice that the first VK3 field day for the coming season will be held to correspond with the VK3 v.h.f. field day held on 28th of September. This is welcome news as it may help with general activity. (Incidentally, it is rumoured that the necessary winning entry for the three VK3 field days—Bob VK3SDX and Wally VK2ZW—was this year splitting up and will be entering the contest under their own names, each being using the same site? Bob has indicated that during every field day to be held in the VK3 area he will be operating on 144, 432 and 578 MHz. from Mt. Buongor, near Ararat, with special emphasis on getting through to VK3SDX on 578 MHz. taking the 2100 Zulu. See report from George VK3QZ.

Melbourne National 1 repeater on f.m. has been shifted from Carlton to Dunn's Hill, near, Danang. This is a welcome move, now expected to be about 130 miles with the possibility of some enhancement from tropospheric effects. The new site has also improved the coverage of the repeater.

George VK3ASV in Morwell continues to be up at the front in v.h.f. activity and has now successfully transmitted and received Amateur

TV to Brian VK3BBD in Traralgon. Peter VK3TR and David VK3ABC, both of Sale, are continuing a.v. gear, while Dave VK3AB is an excellent closed circuit a.v. set-up working, and is currently developing a 432 MHz. tx-rx set-up for a.v.

Bob further advises increased activity in Mildura where there are now at least seven stations operating on six metres. This is good news for their district. The 144 MHz. section in the DX season will give an indication of the rise in the number of skip conditions, indicative of a shortening of the MUF and significant possibility of useful 2 m. contacts. Other 8 m. activity of interest includes contact between Kerry VK3SU at Ceduna and VK3ZCM in Perth on 12th. Leigh VK3JH continues to operate nightly on 33.150 at 1900 and beaming east.

David VK8AU in Tennant Creek sends a letter advising having worked JAEFC and JRJNP on 12th May. His DX log for May and June should be of interest:

15.5-0520—VK8KX on forward scatter.
16.6-1715—JRJMUZ F2
22.3-0500—VK8KX forward scatter & M/S.
5.6-0600—VK3SDXW M/S.
6.0-0630—VK8KX M/S & M/S.
6.6-0700—VK8KX F3 & M/S.
6.6-0830—VK8KX M/S.
0700—VK3SDXW M/S.
0715—VK3SDXW M/S.
9.6-0830—VK8KX M/S.
0700—VK3SDXW M/S.
9.6-1020—VK3SDXW Sporadic E.
10.25-1030—VK3SDXW M/S.
10.6-1070—VK3SDXW M/S.
11.0-1070—VK3SDXW M/S.

David goes on to say "As you can see, 6 m. is never really dead. The signals from VK3SDXW were really good, considering the fact he was running 80 watts p.p. input and a 6 element yagi. The signal was very good. Bob and I was to call alternate five minutes using break-in s.s.b. In this way, if a reply was received, the other station would not be totally exchanged. It is remarkable the amount of information that can be exchanged on a very busy band using this technique. I occasionally hear good bursts from the VK3 beacon VK3VAF on 33.000 MHz.

"Present indications are that for very high power and low loss, a 2.8 m.b. p.p. input range of 1,300 miles is feasible. Signals rapidly improve below this distance to where 300-400w. p.p. e. is useful in the 300 to 1,100 mile range. Below this range, power requirements tend to get more stringent again as we move out of the M/S region into the forward scatter region. Below 300 miles again, power requirements drop off.

"It is not easy to generate 400 watts, p.p. output on 144 MHz. as most linear txs. run at only 50% efficiency once you get above about 30 MHz. Antenna gain figures also tend to be on the optimistic side too, and feedline losses are ALWAYS more than quoted. VK3KX and I both use helix on our 6 m. antennas. Thanks David for your letter and the interesting observations contained therein.

144 MHz. BAND PLAN

The following information has been supplied by George VK3ASV of Morwell and is a band sealing report by the Eastern Zone of VK3. It is to be read as a general guide and not to be taken too literally. It is an attempt to provide a guide to the use of the 144 MHz. band plan in particular. Being in Alice Springs at the moment and with a slight delay in the receipt of an appropriate letter to provide this information. Your thoughts on the matter would be gratefully received by me, and if of sufficient general interest could be included in "Amateur Radio" for others to consider.

"The Eastern Zone last year set up a group to study a 144 MHz. band plan or segment, results outlined and discussed at recent general meetings on 19th Sept., 3rd Dec., 1970, and 10th March 1971. The group has now started to take shape (March 1971).

"In the report the group recommendation is that the 144 MHz. band plan be split into two spot frequencies between 144.400 and 144.496 MHz., thus 18 working channels at 6 kHz. The 144 MHz. band plan is to be too restrictive on the individual operator, he may still v.o. off his working frequency outside the zone segment to net on or to work E. or W. or on a special mode such as moonbounce, meteor scatter, aurora, buck scatter and/or record attempts, etc.

"First consideration is band planning necessary if it is to be useful to anyone. New Zealand as they are currently considering the same thing. Also, near-by countries in case of a.m. or f.m. on existing or stationary (sync.) satellites. Hence we have a conference at Federal or National level to formulate such a plan?

"In drawing up a plan, thought would have to be given to existing services as well as future developments. The plan would be:

144.000 to 144.1—C.W. and DX, international moonbounce experiments, aurora and buck scatter.
144.1-144.5—Free operation, perhaps with some zoning for regions.
144.5-National a.m. mobile net frequency.
144.5-145.0—Experimental beacons.
145.0 to 147.5—F.m. simplex nets (national 146.0), repeaters and translators (linear and simplex).
147.5 to 148.0—Experimental cross-band translators.

"The rest of the band not specifically allocated to being a testing area. Note in New Zealand, 144.65 to 147.75 is used as civil defence and A.R.C.E. nets similar to our W.I.C.E.N., leaving a small portion for free operation except during emergencies. We should therefore use this portion if we don't want to lose it to commercial land-mobile radio-telephone service.

"Finally, the a.m./s.s.b. or lower portion could be further divided regionally where necessary. England has had this for 20 years, in which the whole country followed a band plan supported by the v.h.f. committee of the I.R.S. The plan was divided into four zones. It was implemented into four zones 13 months ago. Here in Australia and New Zealand this sounds attractive and it is. The plan is to have large unused portions in most areas with the possibility that where there is a large population density it would be overcrowded. It is a small idea, but it is a small idea which can be commensurate."

REPEATER NEWS

A new F.R.S. report was prepared during June and sent to those who received the first issue. England has had this for 20 years, in which the whole country followed a band plan supported by the v.h.f. committee of the I.R.S. The plan was divided into four zones. It was implemented into four zones 13 months ago. Here in Australia and New Zealand this sounds attractive and it is. The plan is to have large unused portions in most areas with the possibility that where there is a large population density it would be overcrowded. It is a small idea, but it is a small idea which can be commensurate."

It has been announced that the proposed beacons for Sydney will be installed in New South Wales. The beacons will be on 144.3 MHz, a 6 metre beacon for Townsville (VK4) will be installed on 32.4 MHz, when licensed.

New Zealand has set up a 2 metre band plan for the country. In the draft plan we received, they have made provision for all modes of operation. There are f.m. simplex channels on 144.3, 144.5, 144.7, 144.9, 145.1, 145.3, 145.5, 145.7, 145.9, 146.1, 146.3, 146.5, 146.7, 146.9, 147.1, 331.3, 331.5, 331.7, 331.9, 332.1, 332.3, 332.5, 332.7,

Amateur Radio, August, 1971

BAIL ELECTRONIC SERVICES

(Proprietors: Fred and Jim Bail)

Our business is to cater for the Radio Amateur with SSB equipment and accessories. It is not a sideline. As the sole authorised agent in Australia for the Yaesu Musen Co. Ltd. since 1963, it is our responsibility, and ability, to provide both general and warranty service, in a properly equipped workshop, with a comprehensive range of spare parts.

Personnel, including Interstate Representatives, are active licensed Hams, with business experience. Thus there is familiarity with Amateur requirements, and the value of service is realised.

Sets are checked before sale. A three-conductor AC power cord with 3-pin plugs is installed in place of the twin cord (usually provided on imported equipment).

A protective RF choke, where necessary, is installed at the antenna output socket.



CURRENT YAESU MODELS:

- ★ FT-200 Transceiver, latest version with provision for external VFO connection, and factory installed key click filter. \$350.
- ★ FV-200 External VFO for FT-200. \$98.
- ★ FP-200 Matching AC Power Supply for the FT-200. \$90.
- ★ DC-200 Matching 12V. DC Power Supply for FT-200. \$120.
- ★ FT-101 Transistorised Transceiver, incorporating the latest modifications. \$675.
- ★ FV-101 External VFO for FT-101. \$98.
- ★ FTDX-560 Transceiver, similar to FTDX-400, as produced for the U.S.A. market. Latest model, incorporating modified heterodyne frequencies. \$595.
- ★ FV-400 External VFO for FTDX-400 and 560. \$98.
- ★ FRDX-400 Receiver, de luxe model. \$395.
- ★ FLDX-400 Transmitter. \$395.
- ★ FL2000B Linear Amplifier. \$375.
- ★ FTV-650 Six Metre Transverter. \$160.
- ★ FT-2F Two Metre FM 12V, DC Mobile Transceiver. \$269.
- ★ FP-2 AC Power Supply for FT-2F. \$65.
- ★ FF-50DX Low Pass Filter. \$22.
- ★ Also Matching Speakers, Spare PA Valves, VHF Converters, CW Filters, Antennas, Rotators, and Amateur Station Accessories.

All prices inc. S.T. and our personalised 90-day warranty.

Prices and specs. subject to change without notice.

BAIL ELECTRONIC SERVICES

60 SHANNON STREET, BOX HILL NORTH,
VIC., 3129. Telephone 89-2213

N.S.W. Rep.: STEPHEN KUHL, P.O. Box 56, Mascot, N.S.W., 2020. Telephone: Day 67-1650 (AH 371-5445)
South Aust. Rep.: FARMERS RADIO PTY. LTD., 257 Angas St., Adelaide, S.A., 5000. Telephone 23-1268
Western Aust. Rep.: H. R. PRIDE, 26 Lockhart Street, Como, W.A., 6152. Telephone 60-4379

radioparts

PROPRIETARY LIMITED

CUSTOMER SERVICE



**Distributors
For Australian and
International
Manufacturers . . .**

TEST EQUIPMENT:

**RAPAR • BWD
SWE-CHECK • HORWOOD**

Call and see our big range of test equipment

SEMI-CONDUCTORS:

**TEXAS INSTRUMENTS
FAIRCHILD AUSTRALIA
PHILIPS • DELCO • ANODEON**



**HORWOOD
R.F. TEST INSTRUMENTS**

1971-72 CATALOGUE NOW AVAILABLE, \$3



radio parts

GROUP

562 Spencer St., West Melbourne, Vic., 3003. Ph. 329-7888, Orders 30-2224
City Depot: 157 Elizabeth Street, Melbourne, Vic., 3000. Phone 67-2699
Southern Depot: 1103 Dandenong Rd., East Malvern, Vic., 3145. Ph. 211-6921

OPEN SATURDAY MORNINGS!